
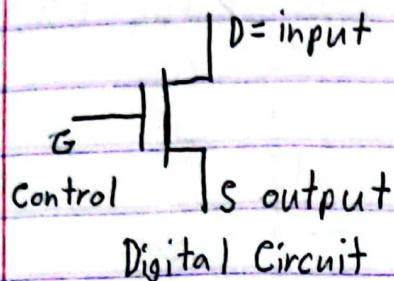


## # MOSFET Device :

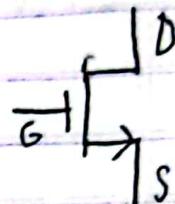


G = Gate  
D = Drain  
S = Source




Analog Circuit

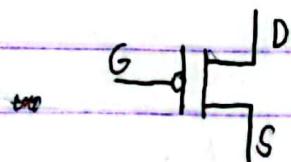- \* It is a transistor.
- \* The Above type of MOSFET are called NMOS.
- \* Another type of MOSFET is PMOS. Its figure;




## # The Switch, S - Model :

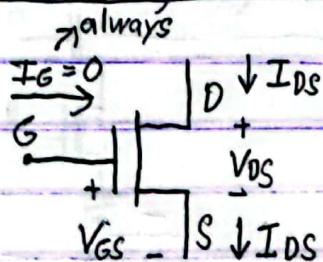


$$V_{DS} = V_D - V_S$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} < V_T$$

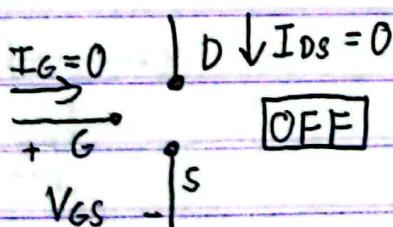


$$V_{GS} \gg V_T$$

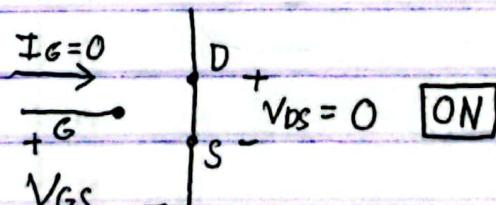


$$* V_T = \text{Threshold Voltage} = 0.5 - 1 \text{ V}$$

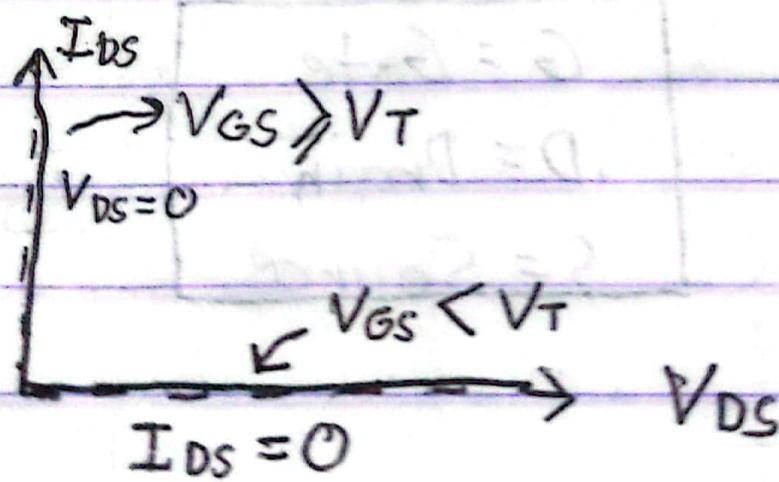- \* If  $V_{GS} < V_T$  then  $I_{DS} = 0$  (Open Circuit)
- \* "  $V_{GS} \gg V_T$  "  $V_{DS} = 0$  (Short " )



# MOSFET logic gates [ $V_T \sim 1V$ ]:

① NOT gate / Inverter:

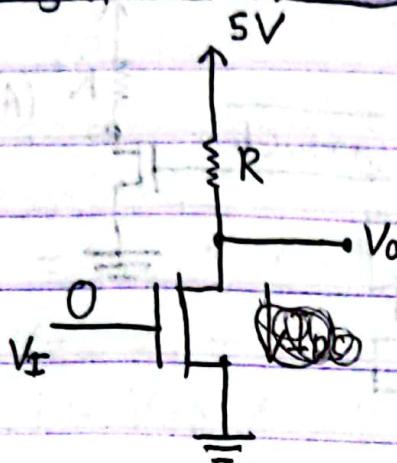


$V_I$	I	$V_o$	O
0V	0	5V	1
5V	1	0V	0

$$V_{GS} \gg V_T \rightarrow S.C$$


$$V_{GS} < V_T \rightarrow O.C$$

② NAND Gate:

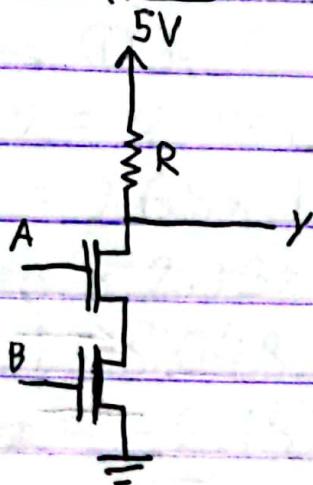

A	B	$y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0


③ NOR Gate:

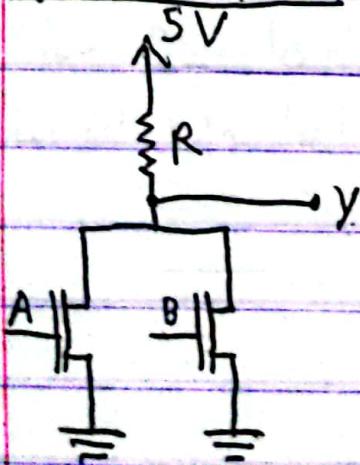


A	B	$y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

# Example:


①  $\overline{AB + C + D}$

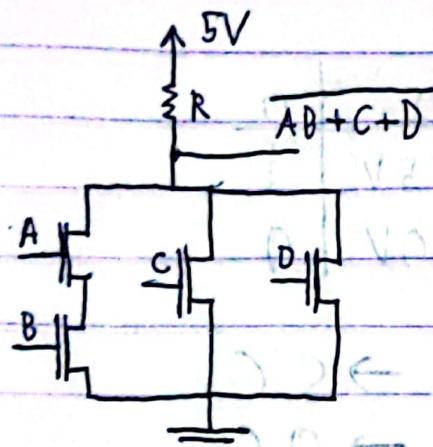

③  $(A+B)CD$

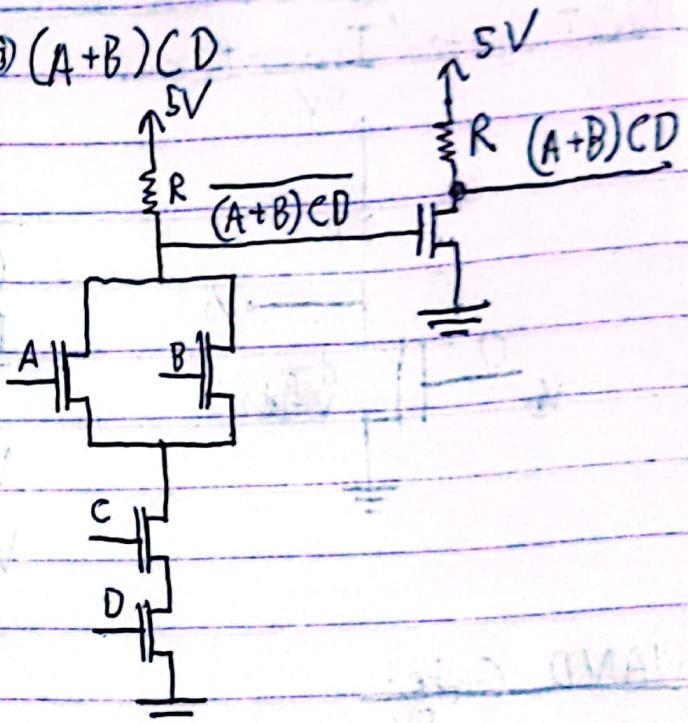


②  $AB + C \overline{(A+B)CD}$

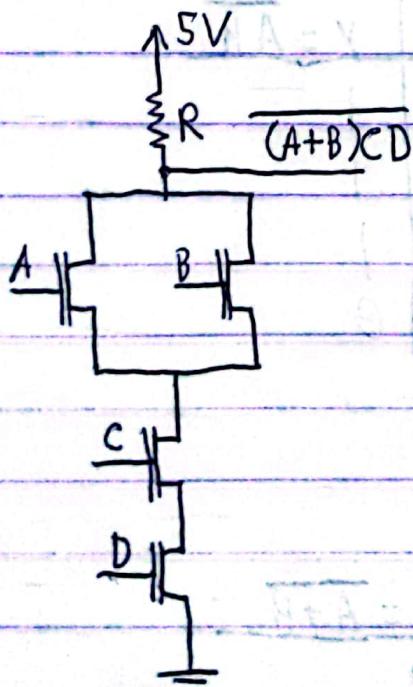

## # Static analysis:

### \* MOSFET Inverter (S-model):

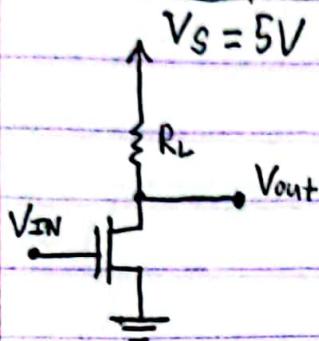


here  $V_{IN} = V_{GS}$


assume  $V_T = 1V$  and  $V_s = 5V$

$$V_{GS} = V_G - V_s = V_G - 5V$$

### \* $V_{IN} < V_T$ :

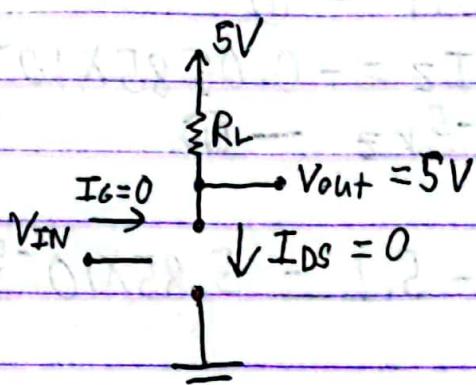

### \* $V_{IN} > V_T$ :

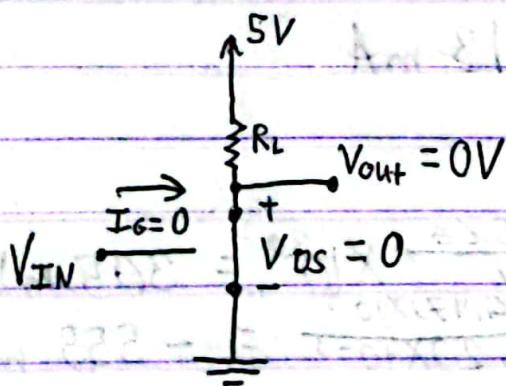

\*  $V_{out}(V)$

$V_s 5V$

$V_{in}(V)$

\* Specification - 1:

$$V_{OH} = 4.5V, V_{OL} = 0.5V, V_{IH} = 4V, V_{IL} = 0.9V$$

- a) Is  $V_{OL} < V_{IL}$ ,  $V_{OH} > V_{IH}$  }  
b) Valid input  $\rightarrow$  Valid output } Conditions to be met

For an inverter,

Input

Valid 0 ( $V_i < V_{IL}$ )  $\rightarrow$

" 1 ( $V_i > V_{IH}$ )  $\rightarrow$

Output


Valid 1 ( $V_o > V_{OH}$ )

" 0 ( $V_o \leq V_{OL}$ )

\* This specification follows static discipline.

\* We cannot change the MOSFET Inverter, we are stuck with what we are given.
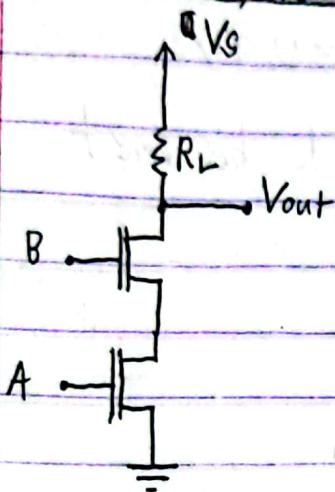
## # Static Analysis of NMOS MOSFET NAND (S-model):



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

\* We can draw the transfer Characteristics graph by considering one input as constant. Like when  $A = 0$  or  $A = 1$ .


\* When  $A = 0$ ,

B	Out
0	1
1	1

When  $A = 1$ ,

B	Out
0	1
1	0
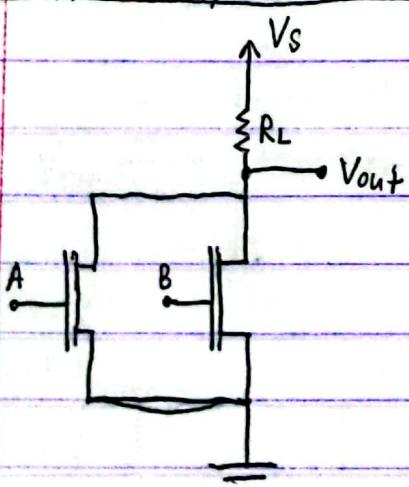
## # State Analysis of NMOS MOSFET NOR (S-model):



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


When  $A = 0$ ,

B	Out
0	1
1	0

When  $A = 1$ ,

B	Out
0	0
1	0


### + The S-model:

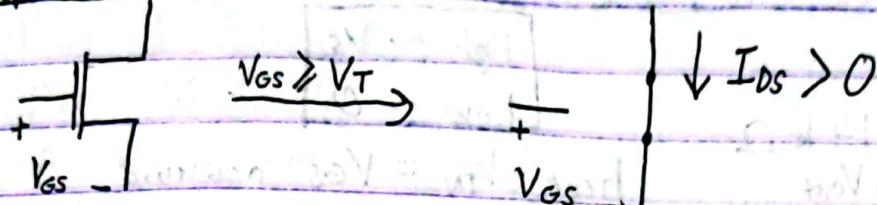

### ① S-Model, ON mode


\* But Material (Si) has non-zero resistance.

### # The SR-Model:

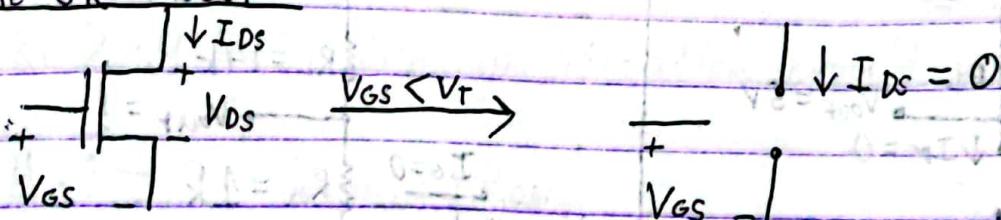

$V_{GS} \gg V_T$
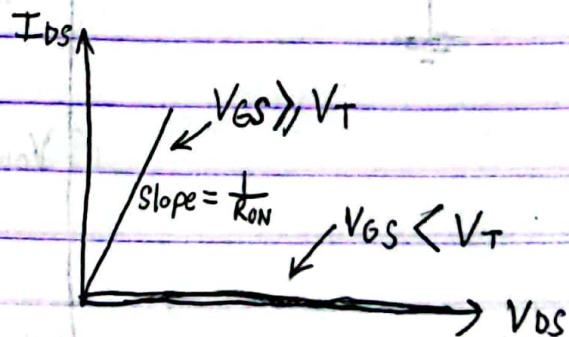
$$R_{ON} = \frac{V_{DS}}{I_{DS}} \quad I_{DS} = \frac{V_{DS}}{R_{ON}}$$




\*  $R_{ON} = \frac{1}{k_n \cdot W \cdot (V_{GS} - V_T)}$  -  $W, L$  = Length and Width of the MOSFET

\*  $V_{GS}$  has 2 values  $V_{GS} = \text{Low}$  and  $V_{GS} = \text{High}$ . Use  $V_{GS} = \text{High}$  for calculating  $R_{ON}$ .

very smaller


This is true only if  $V_{DS} \ll V_{GS} - V_T$  and if  ~~$V_{GS} \gg V_T$~~  it is  $V_{DS} > V_{GS} - V_T$  then it would act like a current source.

## # MOSFET Inverter (SR-model):

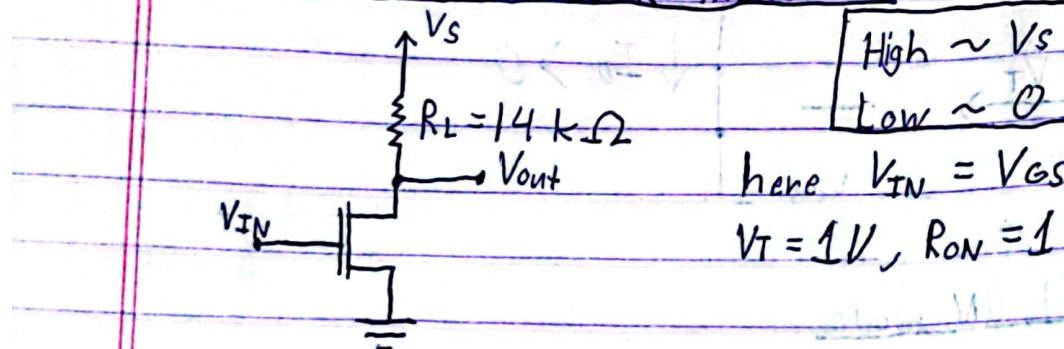


$V_T = 1V$ ,  $R_{ON} = 1k\Omega$  and  $V_s = 5V$

\*  $V_{IN} < V_T$  (Low)

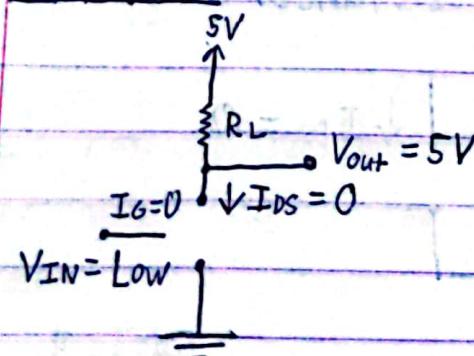

$V_{IN} = \text{High} \geq V_T$

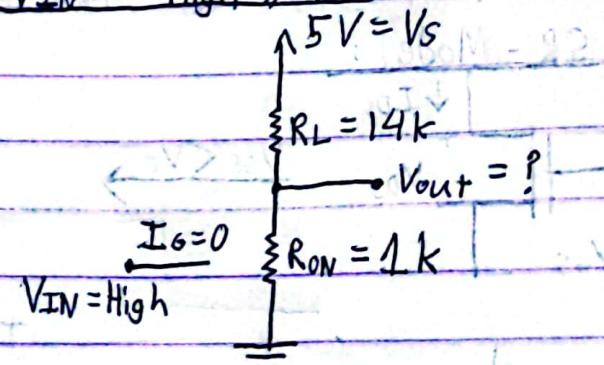

$$V_{out} = \frac{R_{ON}}{R_L + R_{ON}} \times V_s \\ = \frac{1k}{1k + 14k} \times 5 \\ = 0.33V$$

When the input is high,

$\frac{R_{ON}}{R_L + R_{ON}} \times V_s < V_T$  must be maintained.

# To make a specification work we can :  $\frac{R_{on}}{R_{on} + R_L} \times V_s < V_o$

\* Method - 1 : Change  $R_L$

$$\frac{R_{on}}{R_{on} + R_L} \times V_s < V_o$$

$$\Rightarrow \frac{R_{on}}{R_{on} + R_L} < \frac{V_o}{V_s}$$

$$\Rightarrow \frac{R_L + R_{on}}{R_{on}} > \frac{V_s}{V_o}$$

$$\Rightarrow R_L + R_{on} > \frac{V_s}{V_o} R_{on}$$

$$\Rightarrow R_L > \frac{V_s \times R_{on}}{V_o} - R_{on}$$

$$\Rightarrow R_L > \frac{5 \times 1}{0.2} - 1$$

$\Rightarrow R_L > 24 \text{ k}\Omega$  then specification would work.

\* Method - 2 : Change  $R_{on}$

$$\frac{R_{on}}{R_L + R_{on}} \times V_s < V_o$$

$$\Rightarrow R_{on} \times V_s < V_o (R_L + R_{on})$$

$$\Rightarrow R_{on} \times V_s - R_{on} \times V_o < V_o \times R_L$$


$$\Rightarrow R_{on} < \frac{V_o \times R_L}{V_s - V_o}$$

$$\Rightarrow R_{on} < \frac{0.2 \times 14}{5 - 0.2}$$



$$\Rightarrow R_{on} < 0.58 \text{ k}\Omega$$

#

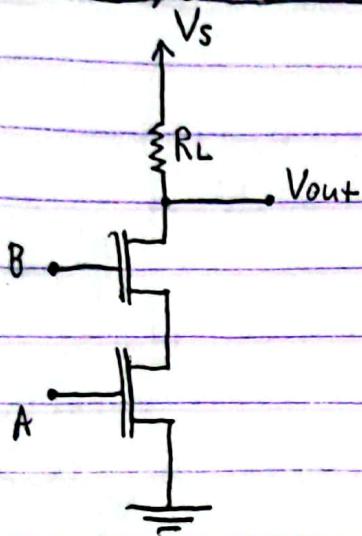
## Static Analysis of MOSFET NAND (CSR-Model):



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

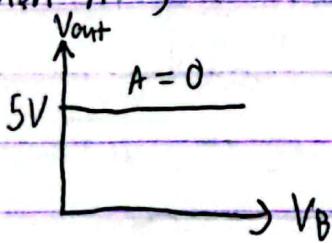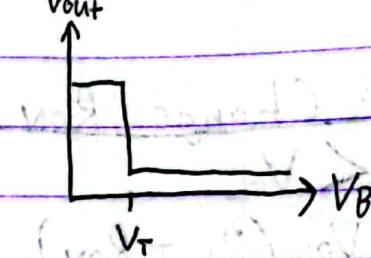
\* When  $A=0$ ,When  $A=1$ ,

$$V_S = 5V$$

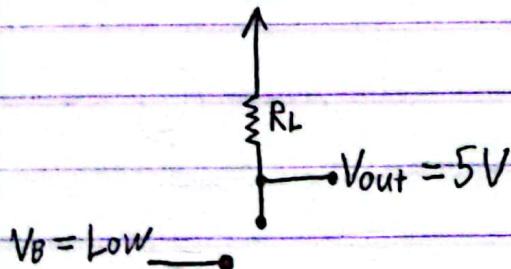

$$V_B = \text{Low}$$

$$V_A = \text{High} \rightarrow R_{ON}$$

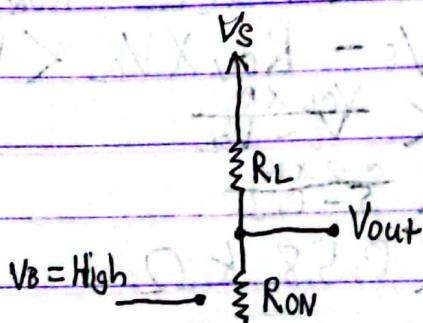


$$V_B = \text{High}$$

$$V_A = \text{High}$$

$$R'_{ON} = 2R_{ON}$$


$$V_{out} = \frac{R'_{ON}}{R'_{ON} + RL} \times V_S$$
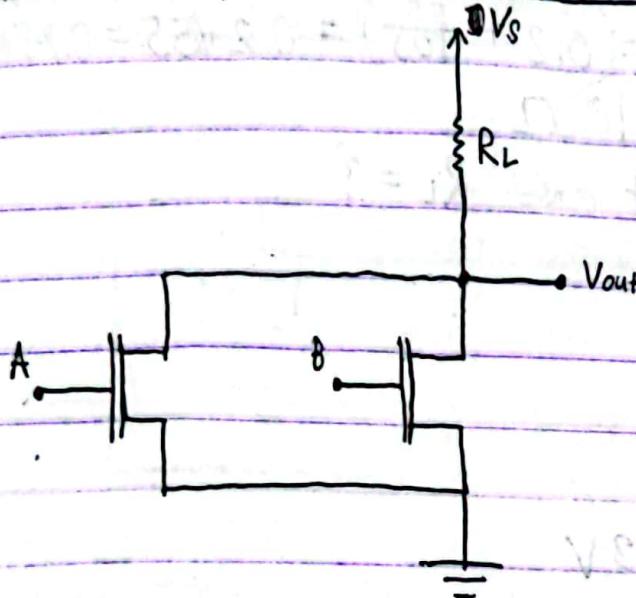
## # Static Analysis of MOSFET NOR (SR-model):




A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


\* When A = Low, B = Low,

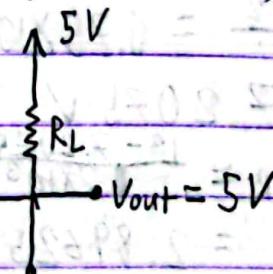


\* When A = Low, B = high,

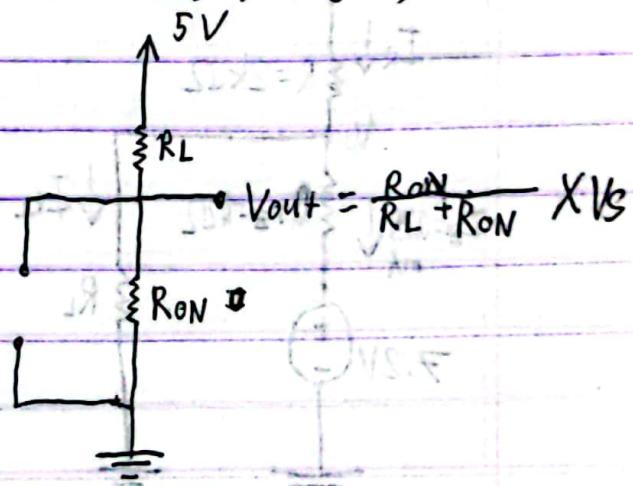


\* When A = High, B = Low

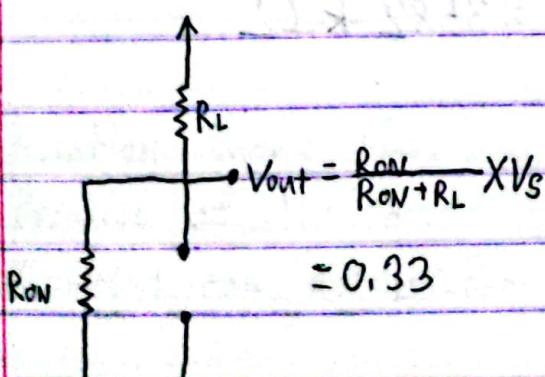

When A = high, B = high,

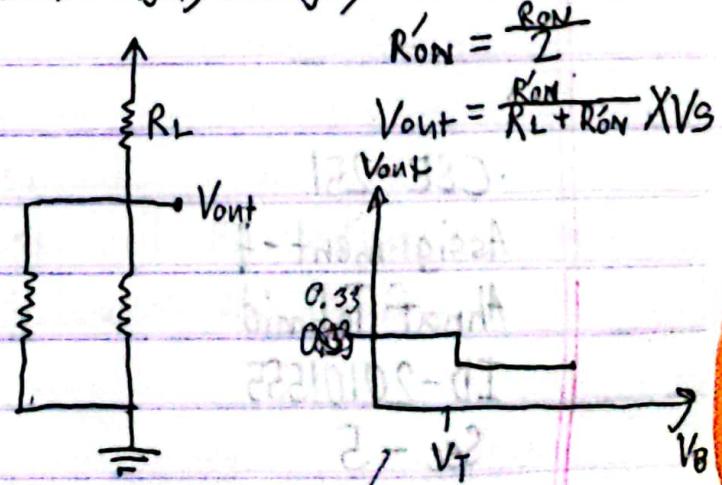

## # Internal Structure of MOSFET:

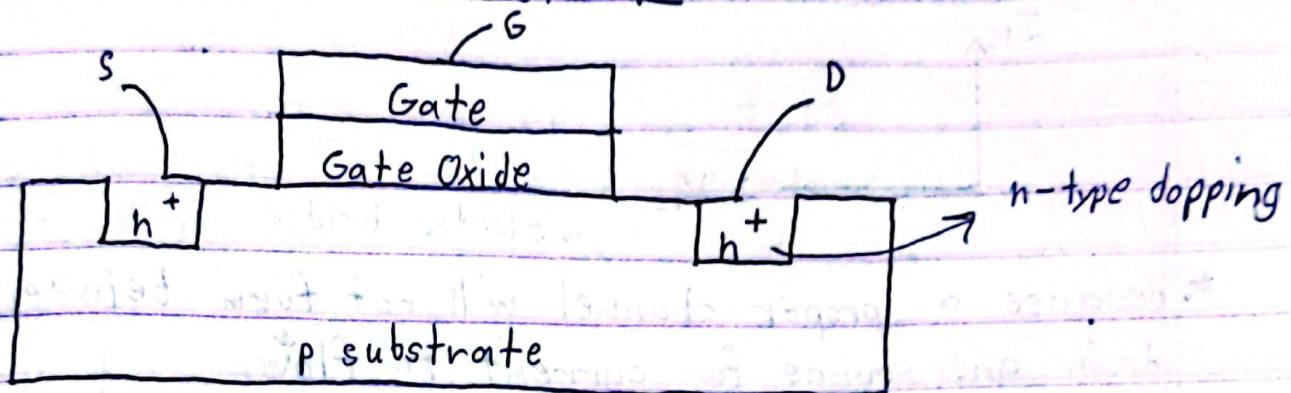


n-type  $\rightarrow$  majority electrons <sup>with</sup> some holes.

p-type  $\rightarrow$  "holes with" electrons.

- \* NMOS is made from p-type substrate as a base.

$$W=10 \text{ (L=15)} (V-2)$$

## # Operation of a MOSFET:

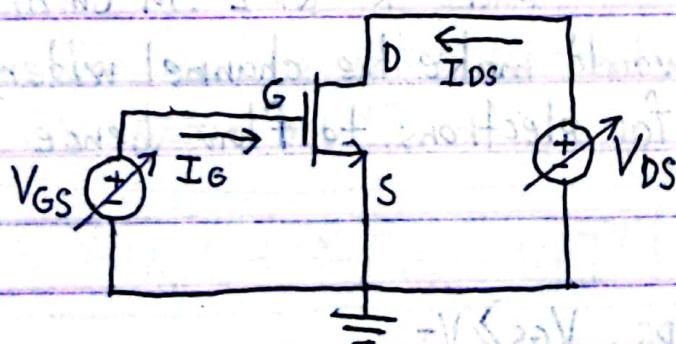


- \* Relation among  $V_{GS}$ ,  $V_{DS}$  and  $I_{DS}$

- \* Because of the oxide layer  $I_{GS}$  will be always  $>$  zero.

- \* Current can never flow from Source to Drain.

\* Case - 1:  $0 < V_{GS} < V_T$

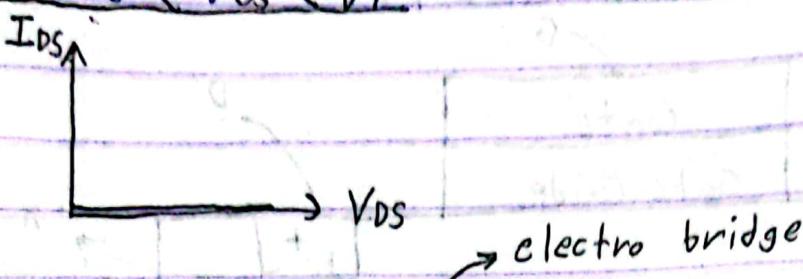


- Because a proper channel will not form between drain and source for current to flow.

\* Case - 2:  $V_{DS} = 0V, V_{GS} \geq V_T$

- Channel will be created for current to flow.

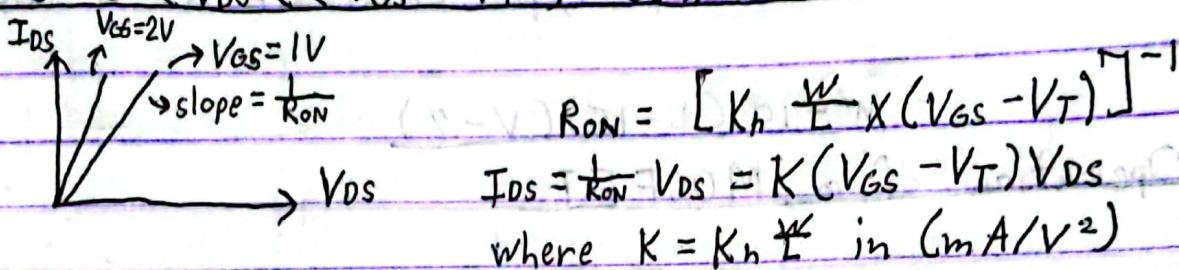\* Case - 3:  $0 < V_{DS} \ll V_{GS} - V_T, V_{GS} \geq V_T$




- Increasing the  $V_{GS}$  would make the channel wider, which would make it easier for electrons to flow hence  $R_{on}$  would decrease.

\* Case - 4: Increased  $V_{DS}, V_{GS} \geq V_T$

- $V_{GS} - V_{DS} \gg V_T$
- $V_{DS} \leq V_{GS} - V_T$
- ∴ If  $V_{DS}$  increase a lot the channel will not remain a flat line hence it will stop current from flowing.
- $V_{GS} = V_T + V_{ov}$  [ $V_{ov}$  = Voltage Overdrive]
- higher  $V_{GS}$  means higher  $V_{ov}$ , and wider the channel will be.
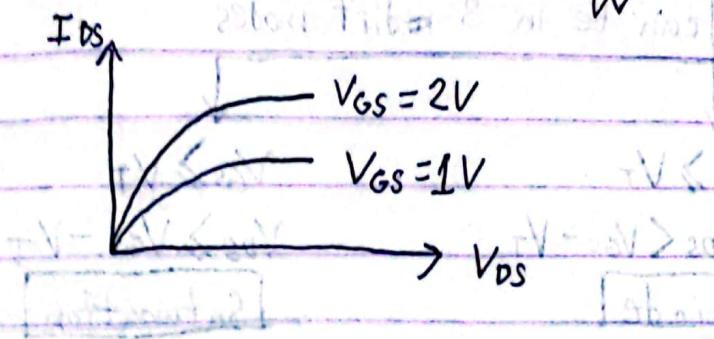
## Continuation of V-2

- But since  $V_{DS}$  is applied  $V_{ov}$  will decrease.
- Voltage diff between  $V_{GS}$  and  $V_D$ ,  $= V_{GS} - V_D = V_T + (V_{ov} - V_D)$
- $\therefore V_{DS} \leq V_{GS} - V_T$  [This mode is called the triode mode of the MOSFET]
- \*  $I_{DS} = K_n \frac{W}{L} [V_{ov} \cdot V_{DS} - \frac{1}{2} V_{DS}^2]$  (will be used more)



The relationship between  $I_{DS}$  and  $V_{DS}$  will non-linear (will be quadratic)


- If  $V_{DS}$  is small, we can ignore  $V_{DS}^2$  ( $\text{mA/V}^2$ )
- \*  $\therefore I_{DS} = K [V_{ov}] V_{DS} = K [V_{GS} - V_T] V_{DS}$ , where  $[K = K_n \frac{W}{L} \text{ in } \text{nA}^{-1} \text{V}^{-1}]$

- \* Case-5:  $V_{DS} = V_{GS} - V_T = V_{ov}$ ,  $V_{GS} \geq V_T$

- The channel will be pinch offed it will look like a triangle shape.
- Current,  $I_{DS}$  can be found by replacing  $V_{DS}$  with  $V_{ov}$ .
- $I_{DS} = K [V_{ov} \cdot V_{ov} - \frac{1}{2} V_{ov}^2]$

$$\Rightarrow I_{DS} = \frac{k}{2} V_{ov}^2 = \frac{k}{2} [V_{GS} - V_T]^2$$


- \* Case-6:  $V_{DS} > V_{GS} - V_T$

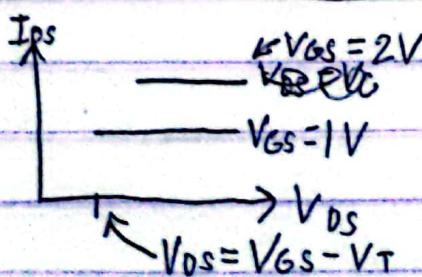

$$I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2$$

- The current is not increasing due to the saturation phenomenon, due to "pinching off of the channel."

## # Summary:

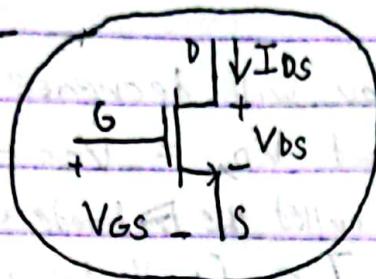

MOSFET

can be in 3 diff modes

$$V_{GS} < V_T$$

**Cutoff**

$$I_{DS} = 0$$

$$V_{GS} > V_T$$

**Triode**

$$0 < V_{DS} < V_{GS} - V_T$$

$$V_{DS} > V_{GS} - V_T$$


**Saturation**

$$V_{DS} > V_{GS} - V_T$$

$$I_{DS} = K [(V_{GS} - V_T) - \frac{1}{2} V_{DS}] V_{DS}$$

$$I_{DS} = \frac{K}{2} [V_{GS} - V_T]^2$$

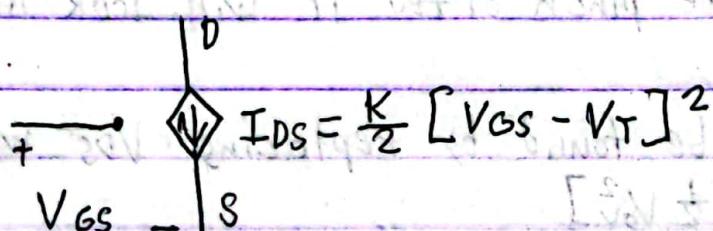- \* In the saturation mode MOSFET will behave like a current source acting like a controlled by  $V_{GS}$ .




- It is not a linear device.

- \* Another condition the MOSFET can have is:

$$V_{DS} \ll V_{GS} - V_T \Rightarrow \boxed{\text{R model}}$$

$$I_{DS} = \frac{1}{R_{ON}} \cdot V_{DS}$$

$$R_{ON} = \frac{1}{K(V_{GS} - V_T)}$$

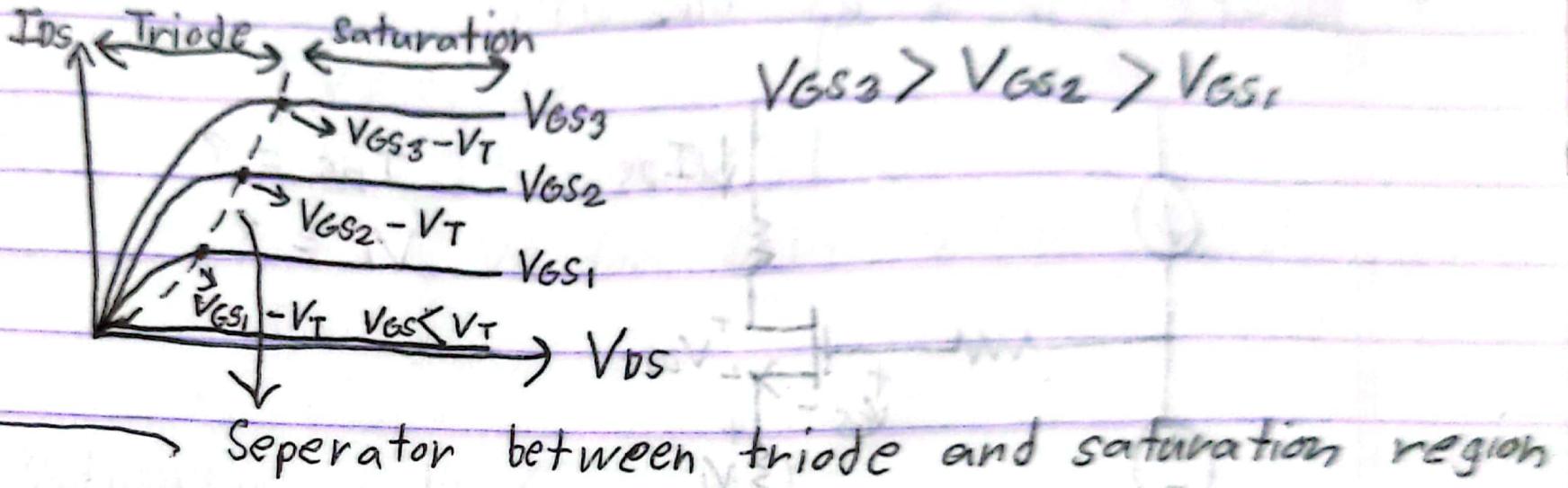


- This threshold is defined as:

$$V_{DS} = V_{GS} - V_T$$

$$I_{DS} = \frac{K}{2} [V_{GS} - V_T]^2$$

$$I_{DS} = \frac{K}{2} \cdot \Phi V_{DS}^2 \rightarrow \text{eqn of the separator.}$$

## # MOSFET in a DC circuit:

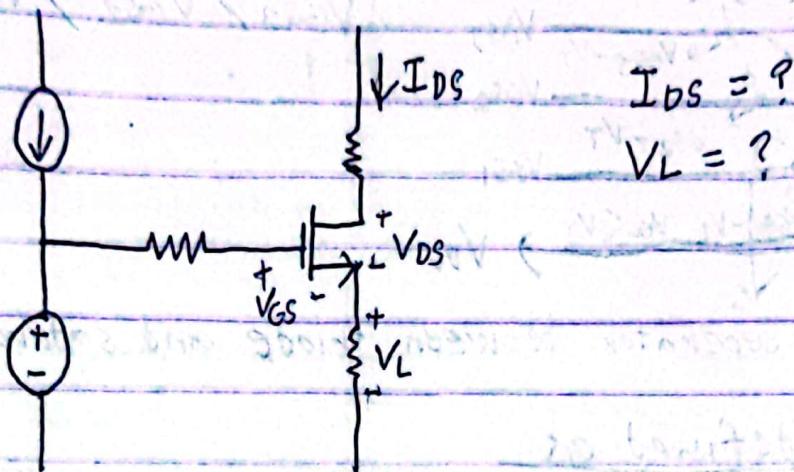

\* We need to use Method of Assumed state to solve it.

① Assume:

Cutoff:  $I_{DS} = 0$

Triode:  $I_{DS} = K[V_{GS} - \frac{1}{2}V_{DS}]V_{DS}$ , where,  $[V_{GS} = V_{GS} - V_T]$

Saturation:  $I_{DS} = \frac{K}{2}[V_{GS} - V_T]^2$

• Start with saturation then triode then Cutoff.

② Solve:

KCL

KVL

③ Verify:


Cutoff:  $V_{GS} < V_T$

Triode:  $V_{GS} \geq V_T$ ,  $V_{DS} \leq V_{GS} - V_T$

Saturation:  $V_{GS} \geq V_T$ ,  $V_{DS} \geq V_{GS} - V_T$

\*  $I_{G0} = 0$  always for MOSFET

# Examples:

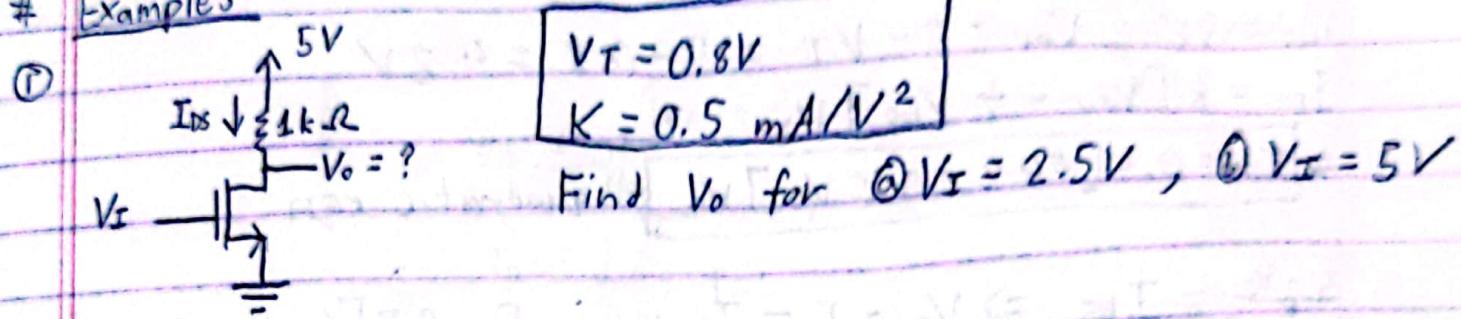

② MOSFET in Saturation mode (assumed)

$$V_S = 0, V_G = V_I = 2.5V, V_{GS} = V_G - V_S = 2.5V$$

$$\therefore I_{DS} = \frac{k[V_{GS} - V_T]^2}{2} = \frac{0.5[2.5 - 0.8]^2}{2} = 0.7725 \text{ mA}$$

$$I_{DS} = \frac{5 - V_o}{R}$$

$$V_o = 5 - I_{DS} \times R = 5 - 0.7725 \times 1 = 4.2275V$$

$$V_{DS} = V_o - V_S = V_o - 0 = V_o = 4.2275V$$

Check:

- $V_{GS} \gg V_T$

$$2.5 \gg 0.8 \text{ (True)}$$

- $V_{DS} \gg V_{GS} - V_T$

$$\Rightarrow V_o \gg V_{GS} - V_T$$

$$\Rightarrow 4.2275 \gg 2.5 - 0.8$$

$$\Rightarrow 4.2275 \gg 1.7 \text{ (True)}$$

} Since both conditions are fulfilled so the assumption is correct.

③  $V_I = 5V, V_{GS} = V_I - V_S = 5V$ , Assume Saturation mode:

$$\textcircled{1} I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2 = \frac{0.5}{2} [5 - 0.8]^2 = 4.41 \text{ mA}$$

$$V_o = 5 - I_{DS} \times R = 5 - 4.41 \times 1 = 0.59V$$

Checking:

- $V_{GS} \gg V_T$

$$5 \gg 0.8 \text{ (True)}$$

•

$$V_{DS} \gg V_{GS} - V_T$$

$$\Rightarrow V_o \gg V_{GS} - V_T$$

$$\Rightarrow 0.59 \gg 5 - 0.8 \text{ (False)}$$

} Assumption is not true.

\* Assume Triode Mode:

$$V_{GS} = 5V, V_{ov} = 5 - V_T = 5 - 0.8 = 4.2V$$

$$I_{DS} = K [V_{ov} - \frac{1}{2} V_{DS}] V_{DS}$$

$$\Rightarrow I_{DS} = 0.5 [4.2 - 0.5 V_o] V_o \quad \text{quadratic eqn}$$

$$\frac{5 - V_o}{R} = I_{DS} \Rightarrow V_o = 5 - I_{DS} \times R = 5 - 0.5 [4.2 V_{DS} - 0.5 V_{DS}^2]$$

$$\Rightarrow V_o = 5 - 2.1 V_{DS} + 0.25 V_{DS}^2$$

$$\Rightarrow 0.25 V_{DS}^2 - 3.1 V_{DS} + 5 = 0 \quad [V_{DS} = V_o]$$

$$\Rightarrow 0.25 x^2 - 3.1 x + 5 = 0$$

$$\Rightarrow x = 1.9V, x = 10.492$$

$$\therefore V_o = 1.9V$$

\* Check:

$$V_{GS} > V_T$$


$$5 > 0.8 \text{ (True)}$$

$$V_{DS} < V_{GS} - V_T$$

$$1.9 < 5 - 0.8 \text{ (True)}$$

\* ∴ Assumption is correct.

#10 Example:

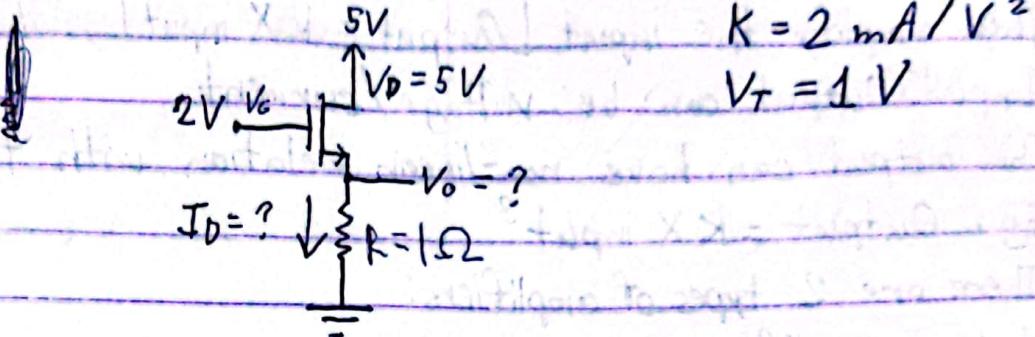

\* Assume Saturation mode:

$$V_{GS} = V_G - V_S$$

$$\Rightarrow V_{GS} = 2 - V_0$$

$$I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2$$

$$\Rightarrow I_{DS} = \frac{2}{2} [2 - V_0 - 1]^2$$

$$\Rightarrow I_{DS} = [1 - 2V_0 + V_0^2]$$

$$I_D = \frac{V_0 - 0}{R} \Rightarrow V_0 = I_D R$$

$$\text{Q1) } V_0 = I_{DS} \cdot X R = I_{DS} \times 1 = 1 - 2V_0 + V_0^2$$

$$\Rightarrow V_0^2 - 3V_0 + 1 = 0$$

$$\therefore V_0 = 2.6 \text{ V and } V_0 = 0.4 \text{ V}$$

$$2 - V_0 > 1 \text{ V} \Rightarrow V_0 < 1 \text{ V}, \therefore V_0 = 0.4 \text{ V}$$

$$\therefore I_{DS} = 0.4 \text{ mA}$$

\* Check:

$$\bullet V_{GS} > V_T$$

$$1.6 > 1 \text{ (True)}$$

$$\bullet V_{DS} > V_{GS} - V_T$$

$$\Rightarrow 5 - V_0 - V_S > V_{GS} - V_T$$

$$\Rightarrow 5 - 0.4 > 1.6 - 1$$

$$\Rightarrow 4.6 \text{ V} > 0.6 \text{ V (True)}$$

$\therefore$  The assumption is ~~True~~ correct.