




Inspiring Excellence

**Name** : Md.Tasnim Muttaki  
**Id** : 21101216  
**Subject** : Digital Electronics  
**Course code** : CSE 251  
**Section** : 02

Q-9

Q1  
1.5  
 $V_{max}$   
 $V_{in}$

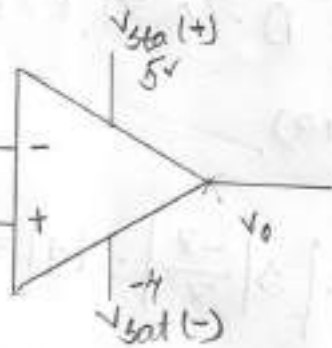

b)




Q-10 Part-1 a)  $R_i = 2\text{ k}\Omega$ ,  $R_F = 10\text{ k}\Omega$ ,  $V_{\text{sat}(+)} = 10$   
 $V_{\text{sat}(-)} = -5$

Now,

$$\frac{-R_i \cdot V_{\text{sat}}^+}{R_F} = -\frac{2 \times 10}{10} = -\frac{20}{10} = -2$$
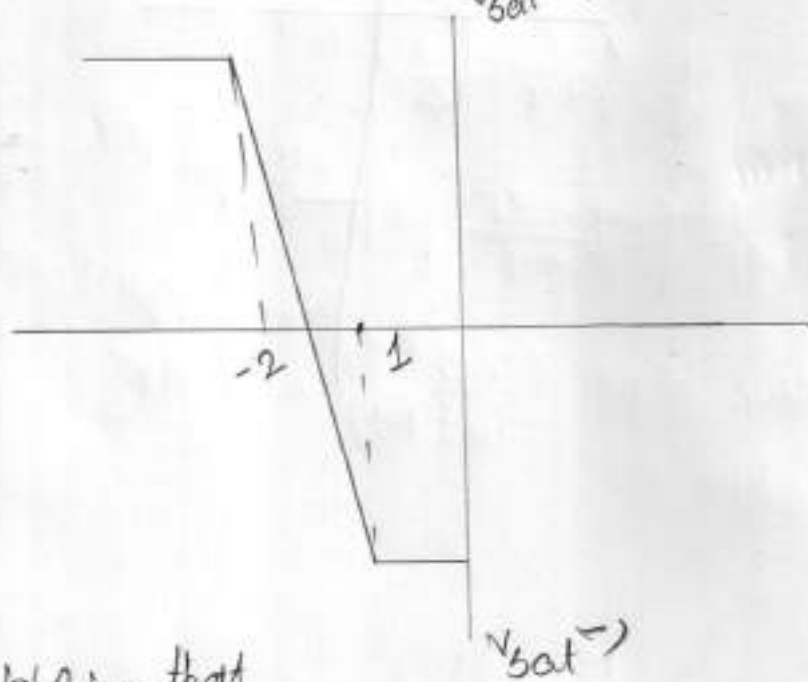
$$\frac{-R_i \cdot V_{\text{sat}}^-}{R_F} = -\frac{2 \times (-5)}{10} = \frac{10}{10} = 1$$



b) Given that

$$V_i = 0.1 \sin(\omega t)$$

$$V_o = -\frac{R_F}{R_i} V_i = -\frac{10}{2} \cdot 0.1 \sin(\omega t)$$

$$= -0.5 \sin(\omega t)$$

Part-2 (e)  $\frac{R_i \times 2}{R_i + R_f} = 4$

$$\Rightarrow 2R_i = R_i + R_f$$

$$\Rightarrow R_i = R_f$$


Again,

$$\frac{R_i \times 3}{R_i + R_f} = 4$$

$$\Rightarrow 3R_i = 4R_i + 4R_f$$

$$\Rightarrow 4R_i = 4R_f$$

$$\Rightarrow R_i = R_f$$

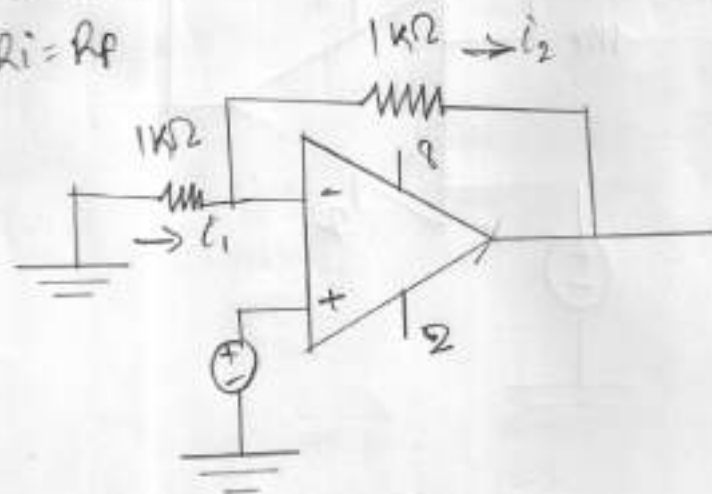


$$\underline{b)} \left(1 + \frac{R_F}{R_i}\right) \geq 1$$

$$\Rightarrow (1+1) > 1$$

$$\Rightarrow 2 > 1$$

$\therefore$  voltage gained.

Q1

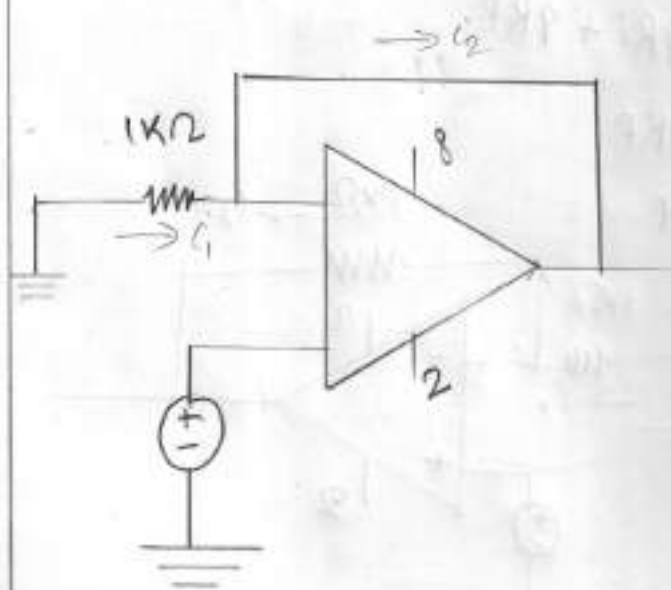


Q-13]

We know,

$$V_o = -RC \frac{dV_i}{dt}$$


$$\therefore \text{Slope} = \left| \frac{dV_m}{dt} \right| = \frac{V_m - (-V_m)}{T/2} = \frac{4V_m}{T}$$
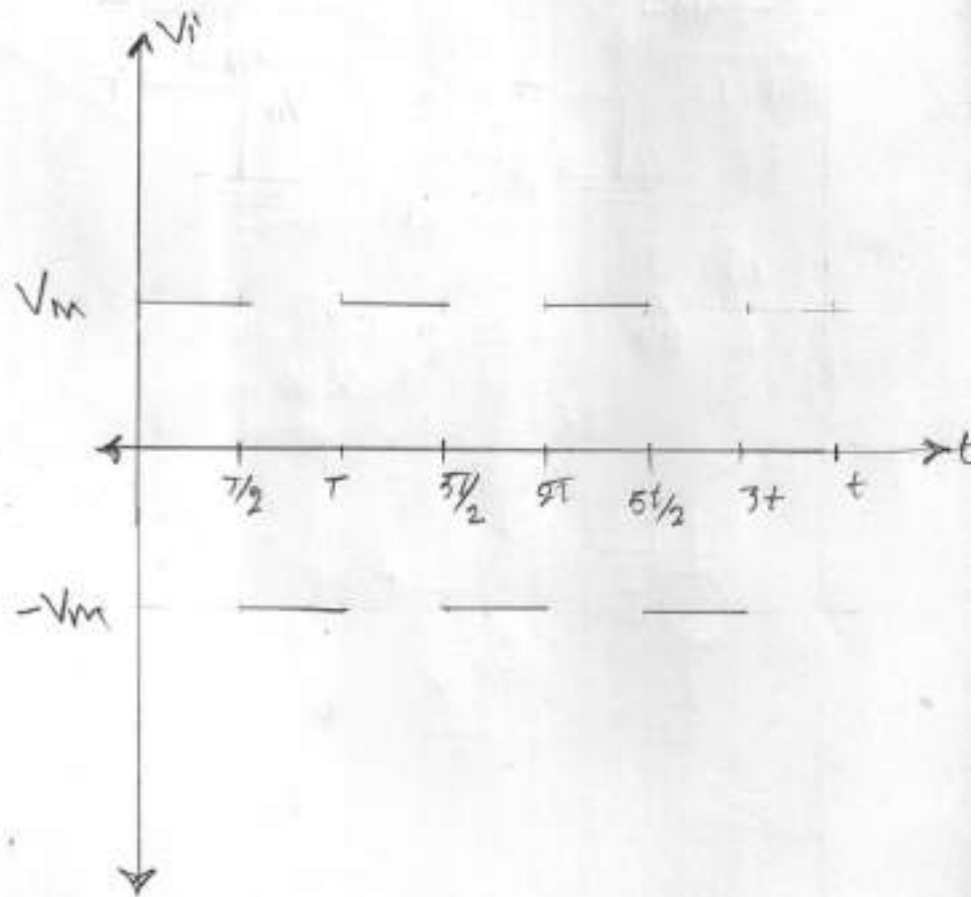
$$\therefore V_{o1} = -RC \frac{4V_m}{dT}, \quad V_{o2} = RC \frac{4V_m}{T}$$



Q-15)

$$V_o = 6V_1 - 10V_2 + 4V_3$$

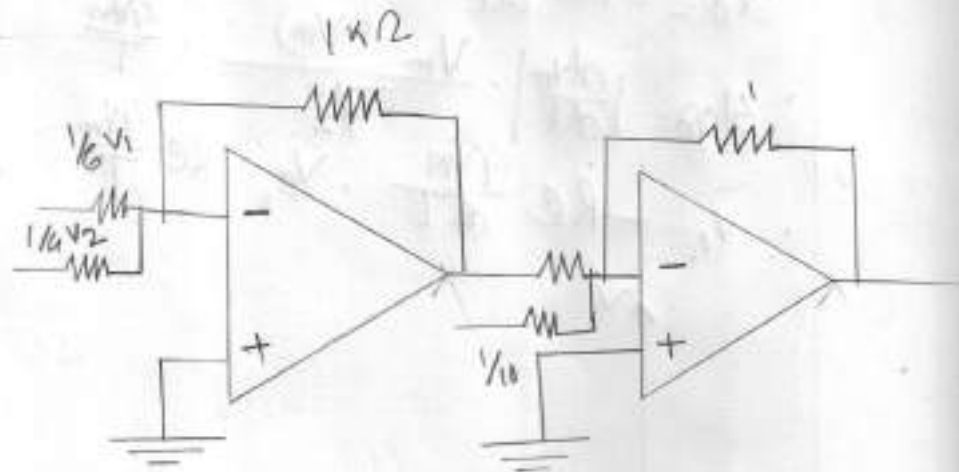

Q-2 (1)

Given that,  $h = 10 \text{ m}$ ,  $P = h \rho g$

Now,

$$P = 10 \times 1000 \times 9.8 = 98000 \Rightarrow 0.96 \text{ atm}$$
$$= \frac{98000}{1.013 \times 10^5} = 0.96718$$

Hence,

in 0.5 atm voltage changes  $\frac{2.5 \text{ V}}{0.5} = 5 \text{ V}$

Now,


in  $(0.967 - 0.5) \text{ atm}$  voltage change  $(0.967 - 0.5) \times 5 = 2.335$

$$\therefore \text{Voltage at } 0.967 \text{ atm} = -5 + 2.335$$
$$= -2.665 \text{ V}$$


$\therefore$  High pressure  $\rightarrow$  high input  $\rightarrow$  valve open  $v^- = 1 \text{ V}$   
low pressure  $\rightarrow$  low input  $\rightarrow$  valve close  $v^+ = 6 \text{ V}$



∴ the Op-Amp given is

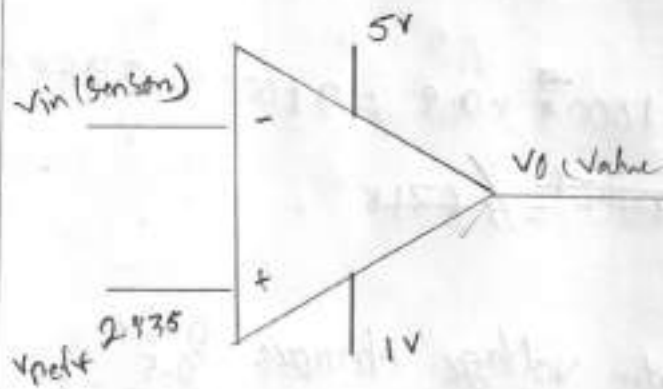

∴  $v_{Te}$  will be

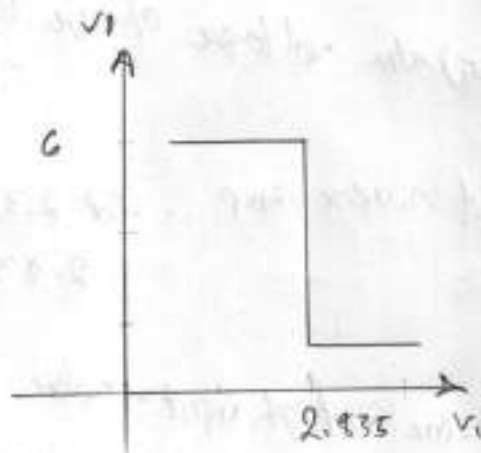

Q-3/ a) Here non-inverting is grounded so the voltage will be  $V_+ = 0V$ , because the inverting node is connected to the feedback it will act as a virtual ground. That's why voltage will be  $V_- = 0V$ .

The relation between  $I_1$  and  $I_2$  is:

$$I_1 = \frac{V_1 - 0}{R} \Rightarrow \frac{V_1}{R} = I_2$$

$$\therefore I_1 = I_2$$

∴ Here,  $\frac{V_1}{R} = C \times \frac{d(V_0)}{dt}$

$$\Rightarrow \frac{V_1}{R} = C \times \frac{d(0 - V_0)}{dt}$$

$$\Rightarrow \frac{d}{dt} V_0 = -\frac{1}{RC} V_1$$

$$\therefore V_0 = -\frac{1}{RC} \int V_1 dt$$

Q1 Given that,


$$R = 10 \text{ k}\Omega, C = 0.1 \mu\text{F}, t = 1 \text{ ms}$$

We know,

$$V_o = -\frac{1}{RC} \int V_i dt$$

$$= -\frac{1}{RC} \cdot V_m \cdot t = -\frac{1 \times 2}{2 \times 10^3 \times 0.1 \times 10^{-3}}$$

$$= 1 \text{ V}$$

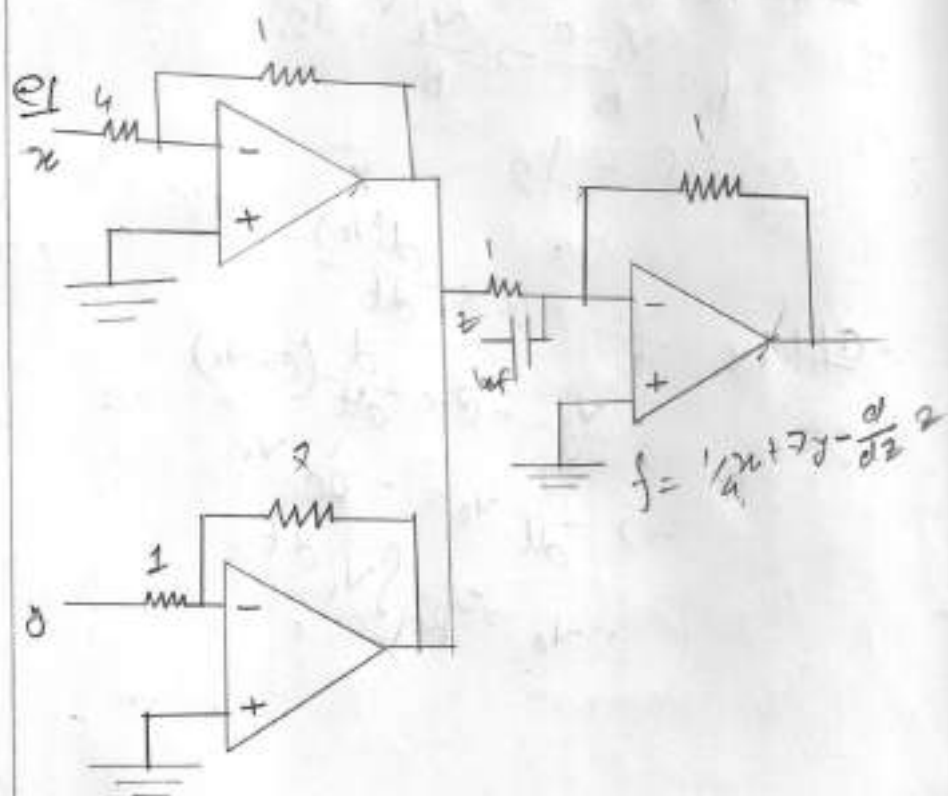

Q-11/

1) We know.

$$y = mx + c$$

$$\text{Now } I = mV_o = \frac{V_o}{R}$$

(ii) Given that


$$V_o = 10\text{V}, R = 3\text{k}\Omega$$

$$\therefore \text{slope } |m| = \frac{1}{3}$$

$$\therefore x\text{-axis } V_o = -10\text{V}$$

$$\therefore y\text{-axis } c = -\frac{V_o}{R} = -\frac{(-10)}{3} = \frac{10}{3}\text{mA}$$

Ans

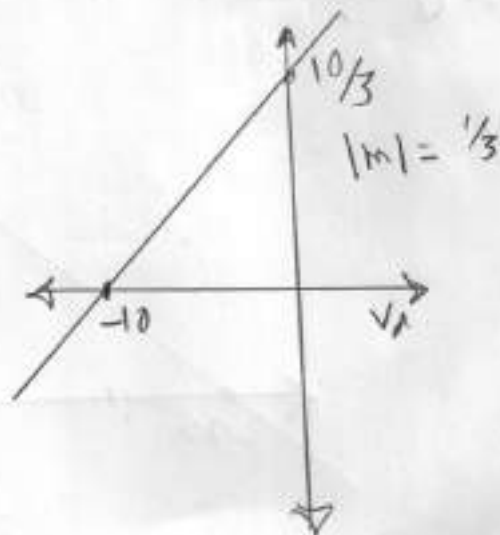

Q-12/1) ∴ Equation of representing curve

$$y = mx + c$$

$$\Rightarrow I = \frac{V_s}{R} + I_0$$

(ii) Given that,

$$V_0 = 10V \quad R = 5k\Omega$$

$$\therefore |m| = \frac{1}{5}$$

∴ x axis


$$\therefore R = -V_0$$

$$\Rightarrow -V_0 = -5 \times 5$$


$$\Rightarrow -V_0 = -25V$$

$$\therefore y \text{ axis} = -I_0 = 5mA$$

(iii)

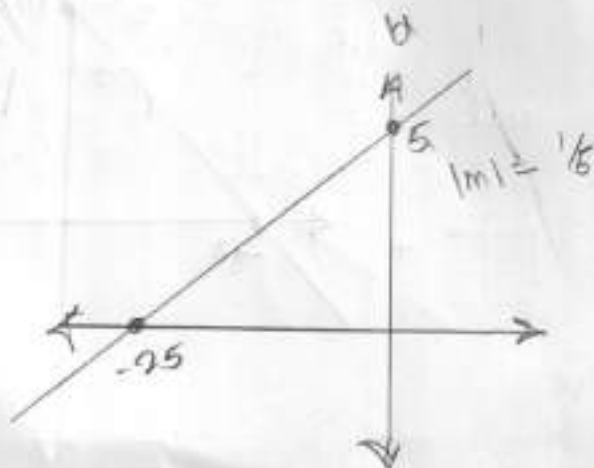

Q-21

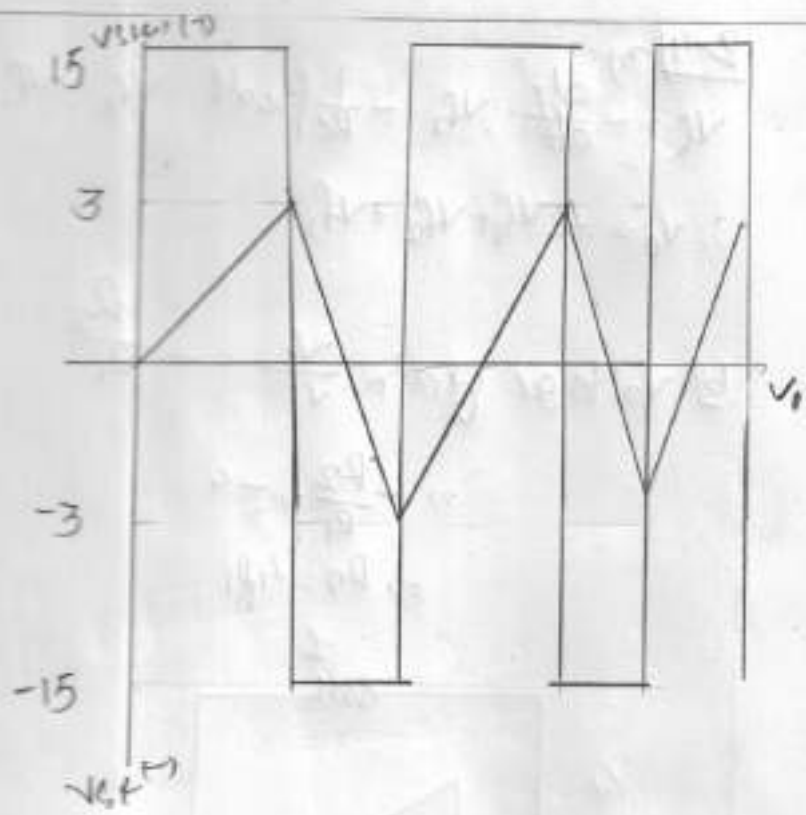


$$2-4) \text{ (c)} \quad v_{f1} = -\frac{dI_1}{dt}, \quad v_{f2} = -\frac{1}{R_2} \int x_2 dt, \quad v_{f3} = -v_{f1} = \frac{dI_1}{dt}$$

$$\therefore v_o = -v_{f1} + v_{f2} + v_{f3}$$

$$\text{b) Voltage gain } \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

$$\Rightarrow -\frac{R_2}{R_1} = -4$$

$$\Rightarrow R_2 = 4R_1$$

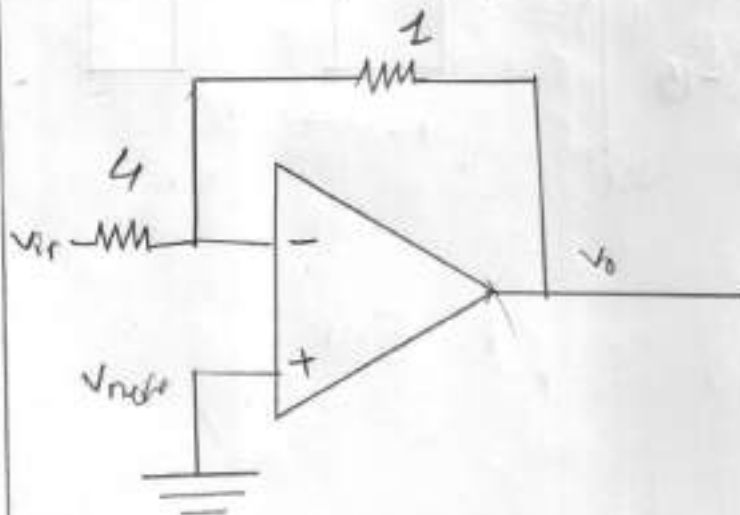

c/ let.  $v_i = 0.5 \sin \omega t$

$$v_o = K v_i$$

$$= 4$$

Amplitude = 1

$$v_o = |K| \times 0.5$$



$$= 4 \times 0.5 = 2V$$

d/ let.  $v_i = 0.5 \sin \omega t$

$$v_o = -4 v_i$$

$$\Rightarrow v_o = -4 \times 0.5 \sin \omega t$$

$$\Rightarrow v_o = -2 \sin \omega t$$

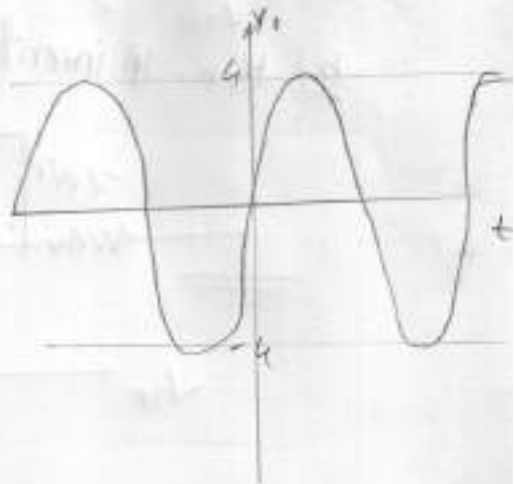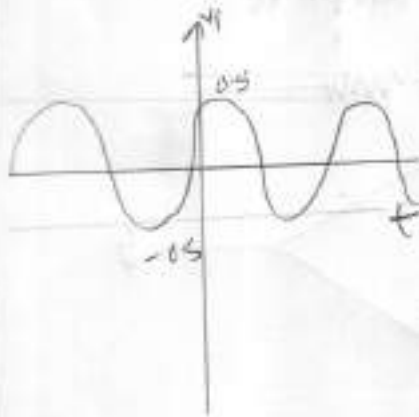




$$Q-5) V_1 = -\frac{1}{R_1 C_1} \int \sin \omega t$$

$$V_2 = R_2 C_2 \frac{dV_1}{dt} \Rightarrow R_2 C_2 \frac{d}{dt} \left\{ -\frac{1}{R_1 C_1} \int \sin \omega t dt \right\}$$


$$V_0 = -\frac{R_3}{R_3} (V_1 + V_2)$$

$$V_1 = -\frac{R_3}{R_3} \left\{ -\frac{1}{R_1 C_1} \int \sin \omega t dt + R_2 C_2 \frac{d}{dt} \left\{ -\frac{1}{R_1 C_1} \int \sin \omega t dt \right\} \right\}$$

Q-6) a) Inverting amplifier

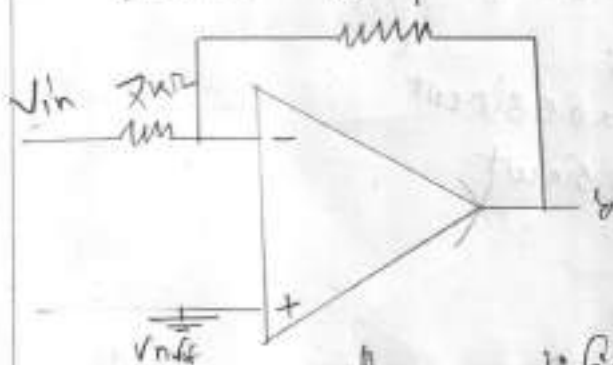

b) Non-inverting amplifier

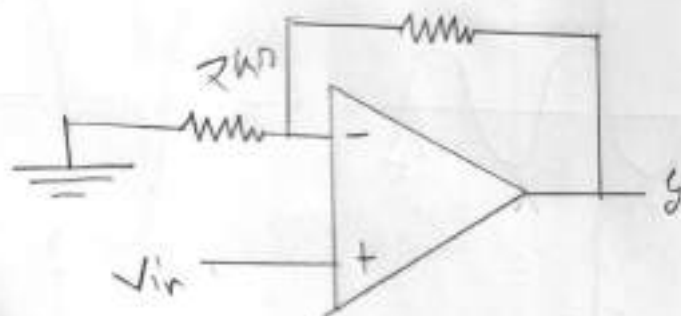

$$\frac{Q}{C_1} V_{f1} = -\frac{1}{4} x_0, \quad V_{f2} = -\frac{dy}{dt}, \quad V_{f3} = -\int q dz$$

$$V_{f2} = -(-\int 2e^{kt}) = \int 2e^{kt} dt$$

$$V_i = -(V_{f2} + V_{f1} + V_{f3})$$

$$V_i = -\left(-\frac{1}{4} x_0 + \int 2e^{kt} dt - \frac{dy}{dt}\right)$$

$$b) V_i = -4V_o$$

$$\Rightarrow -4 = -\frac{R_2}{R_1}$$



$$\Rightarrow R_2 = 4R_1$$

$$\therefore V_o = -4V_i$$

c) Let,

$$V_i = k \sin \omega t$$

$$V_o = -4k \sin \omega t$$

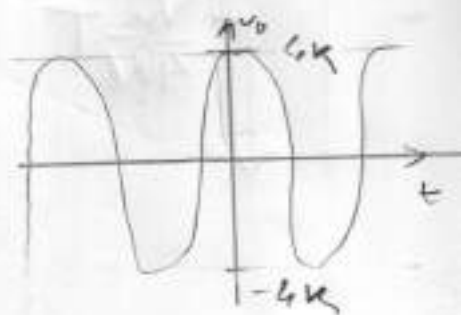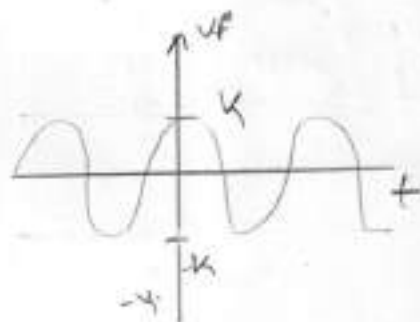

$$d) R_1 = \frac{0.1}{4 \times 10^{-3}} = 25 \text{ k}\Omega$$

$$R_2 = -A_{OL} R_1$$

$$= -(5) \times 25 = 100 \text{ k}\Omega$$

$$(10, V_m) \quad (R_2 = 0) \quad t_{1/2} = \frac{V_i \cdot V_m}{V_m}$$

$$\frac{t-0}{0-T/2} = \frac{V_i - V_m}{V_m - 0} \quad V_i - V_m = \frac{t V_m}{-T/2} \quad V_i = \frac{2+V_m+V_m}{-T} \Rightarrow V_m (-\frac{2}{T} + 1)$$

Q-14)  $V_i = V_m (-\frac{2}{T})t + V_m$


$$V_i = (-\frac{2V_m}{T})t + V_m$$

$$V_i = -\int_{Re} |V_i(t)| dt = -\int_{Re} \left( (-\frac{2V_m}{T})t + V_m \right) dt$$

$$= -\int_{Re} \left[ \frac{V_m T}{4} + \frac{1}{2} V_m T \right]$$

$$V_o = -\frac{V_m}{4Re} T$$

$$-\frac{V_m \cdot T}{4Re}$$

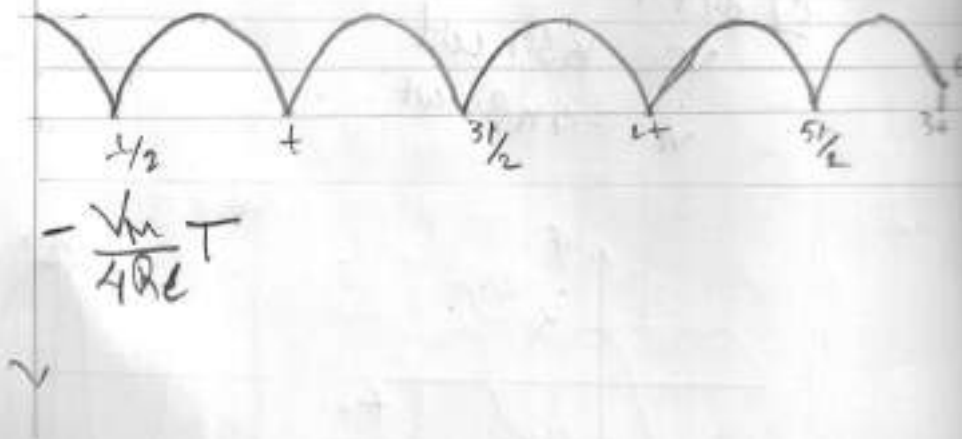

Q-8 | Given that  $D = (0, 7)$ ,  $E = (7, 0)$ ,  $C = (0, -4)$

$A = (-4, 0)$ ,  $B = (-4, 7)$

Now

$$|m_{DE}| = \left| \frac{0-7}{7-0} \right| \Rightarrow \left| \frac{-7}{7} \right| = |-1| = 1$$

$$|m_{CD}| = \left| \frac{-4-7}{0-7} \right| \Rightarrow \left| \frac{-11}{-7} \right| \Rightarrow |1.571| = 1.571$$

$$|m_{AD}| = \left| \frac{7-0}{-4+4} \right| \Rightarrow \left| \frac{7}{0} \right| = \infty$$

$$|m_{BE}| = \left| \frac{-4-7}{0+4} \right| \Rightarrow \left| \frac{-11}{4} \right| \Rightarrow 1.571$$

Here slope  $CD$  &  $BE$  are equal, and  
slope  $AD$  is infinity and slope  $DE$  is negative