
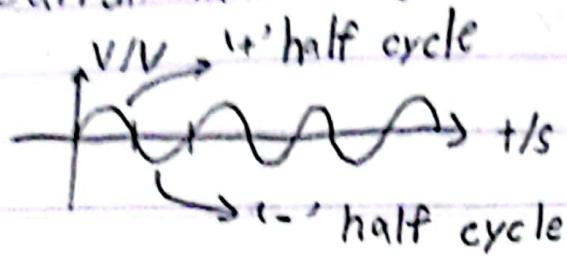


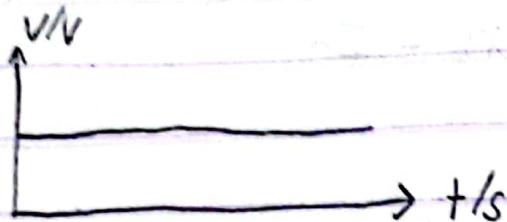
* AC \rightarrow Current that changes direction.



* DC \rightarrow Current's direction stays the same



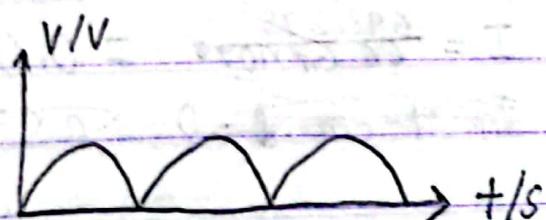* Pulsating DC \rightarrow Current that has 1 direction but different magnitude over time.




* Conversion of AC to pulsating DC is called Rectification.

- Step - 1: Rectification (Converts AC to Pulsating DC).
- Step - 2: Filtering (Reduces variation in magnitude). ^(smoothing)
- Step - 3: Regulation (Decreases variation even more).

1 - 5 (P - 2)


S - transistors

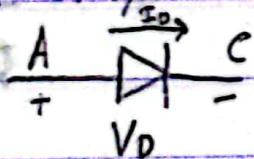* Electronic valve allows current to flow in one direction only.




$$V_D = V_A - V_C$$


* (Forward bias)

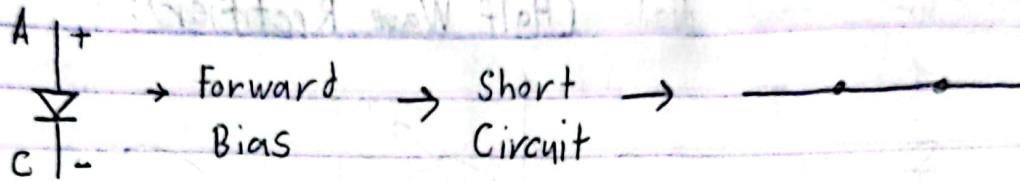

* (Reverse bias)

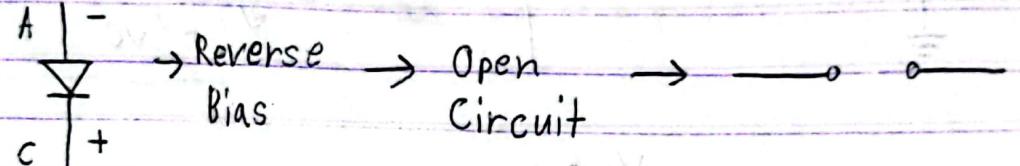

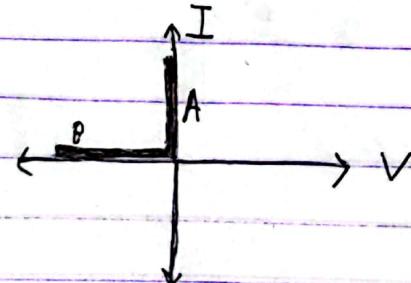* I-V Characteristic of Electronic valve / Diode :





Region - A : F.B, $I > 0$, Short Circuit,

$$V = 0$$





Region - B : R.B, $V < 0$, Open Circuit,
 $I = 0$

L-5 (P-3)

* Line diagram :

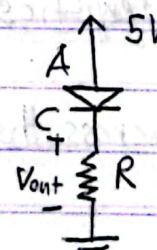
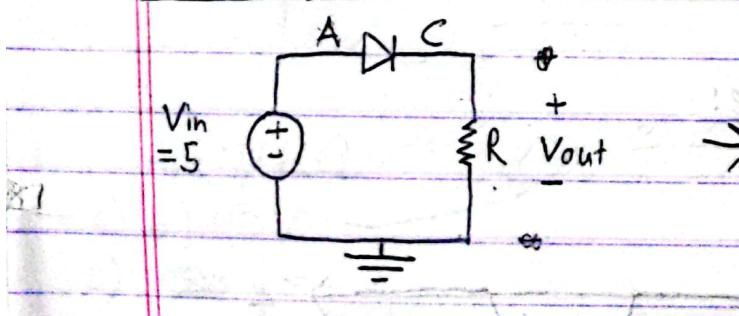


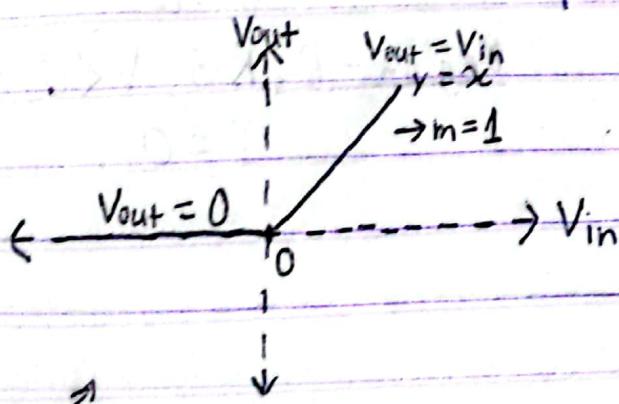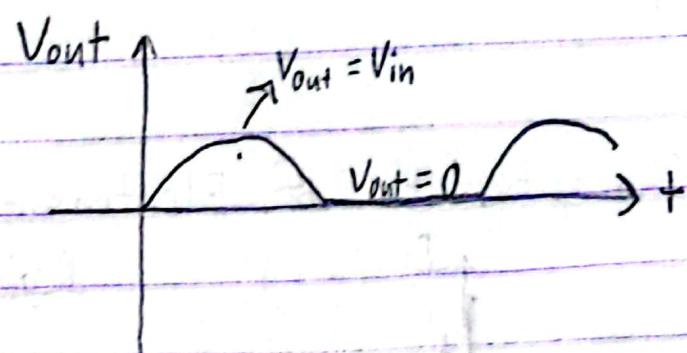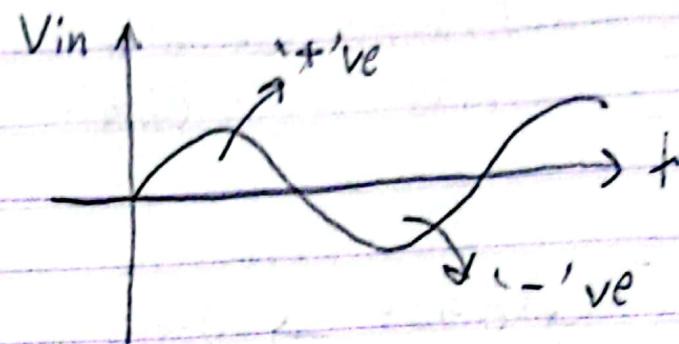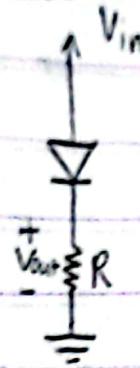AC - source and diode: (Half Wave Rectifier):



Transfer Characteristics

* To find voltage across the diode:

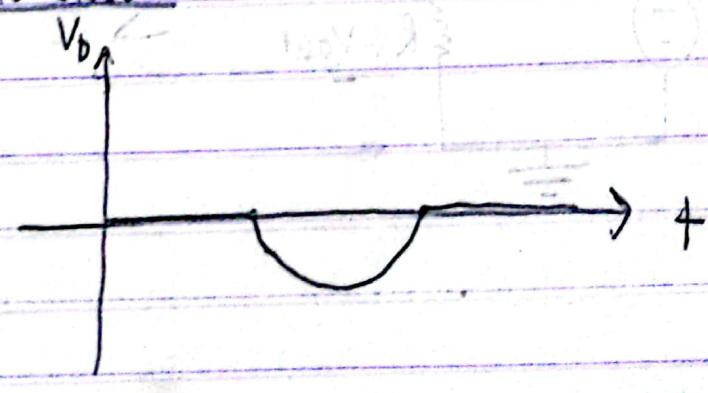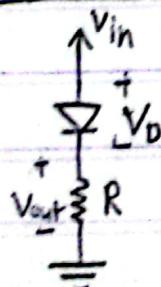

$$V_{in} = V_D + V_{out} + 0$$

$$\Rightarrow V_D = V_{in} - V_{out}$$

Logic Gates:

* Diodes can be used to represent 2 Logic gates:

1) AND gate - 1 only when all inputs are 1

2) OR gate - 0 " " " 1 " 0

* Logic Levels:

$0 \rightarrow \text{False}$ } will be represented
 $1 \rightarrow \text{True}$ } with voltage

$0 \rightarrow 0V / -5V / +12V$
 $1 \rightarrow 5V / +5V / -12V$

this course
this will be used in


W-4 (L-6) (P-3)

OR Operation with Diode:

* Logical truth table:

x_1/V_1	x_2/V_2	y/V_y
0/0V	0/0V	0/0V
0/0V	1/5V	1/5V
1/5V	0/0V	1/5V
1/5V	1/5V	1/5V


* OR Gate Implementation:

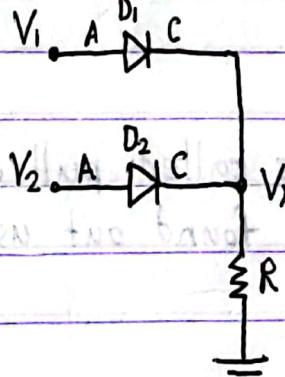

* For current to flow through 'R' $V_y > 0$.



* " diode to be in 'ON' state $V_A > V_c$. If $V_A \leq V_c$ diode is 'OFF'

* Eg: ($V_1 = V_2 = 0$)

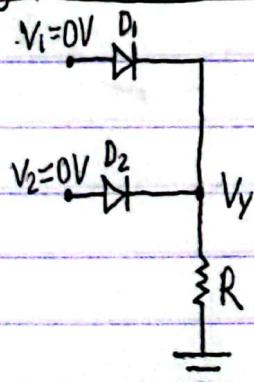


• Since For D_1 , $V_A \leq V_c$, $\therefore D_1 = \text{OFF}$
 and " D_2 , $V_A \leq V_c$, $\therefore D_2 = \text{OFF}$

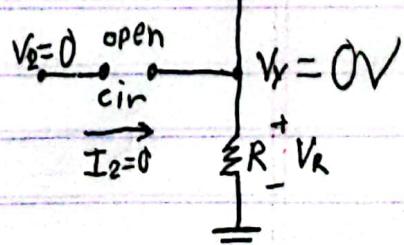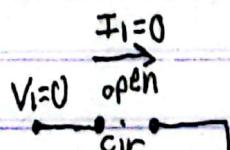
$$\begin{aligned} \therefore \text{Since } V_1 = 0 \text{ and } V_2 = 0, \\ V_y = 0. \therefore V_R = V_y - 0 \\ = 0 - 0 = 0V \end{aligned}$$




* Eg: ($V_1 = 5V = V_2$)

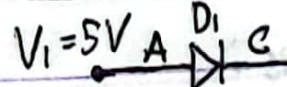

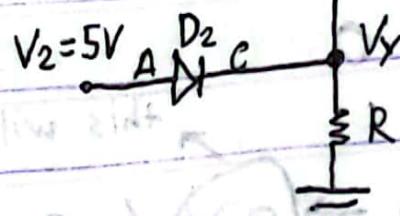D₁:
 $A = 5V, C = 0V, \therefore D_1 = ON$



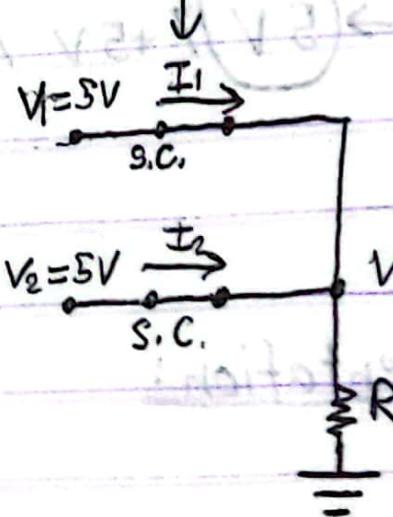D₂:
 $A = 5V, C = 0V, \therefore D_2 = ON$
 $\therefore V_x = 5V$



$$(8-4)(2-1) P = N$$


* The resistor, R is called pull down resistor.

* Max Voltage can be found out using this OR gate implementation.


AND operation with Diode:

* Truth Table:


V_1	V_2	V_y
0V	0V	0V
0V	5V	0V
5V	0V	0V
5V	5V	5V

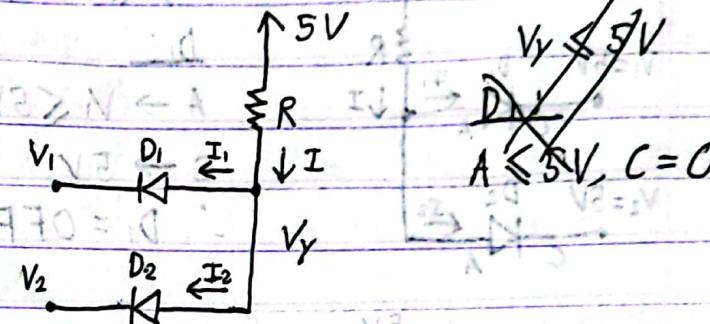


* E.g.: ($V_1 = V_2 = 0V$)

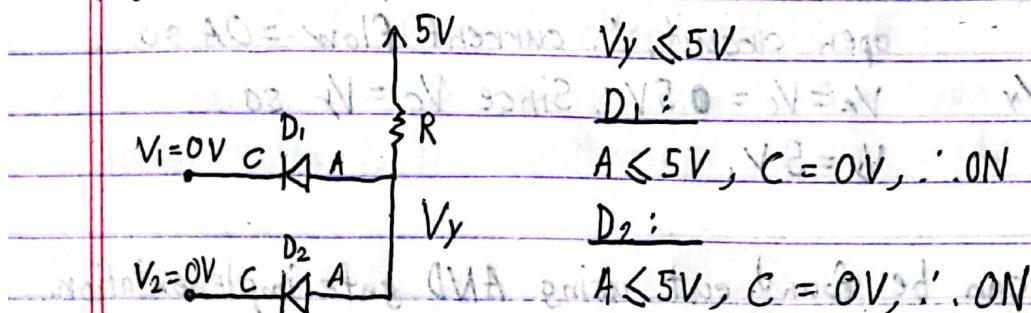

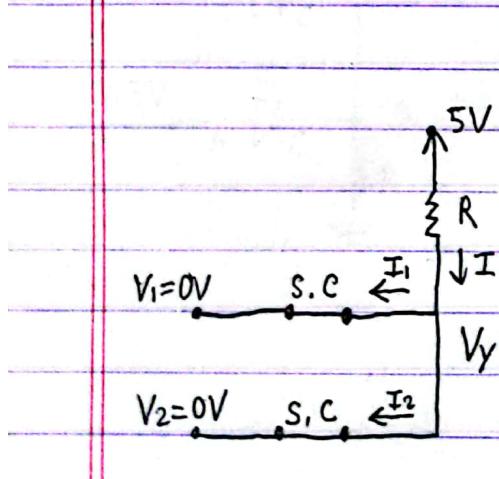• Due to the short circuits $V_1 = V_2 = V_y = 0V$



* $Eg: (V_1 = 5V = V_2)$

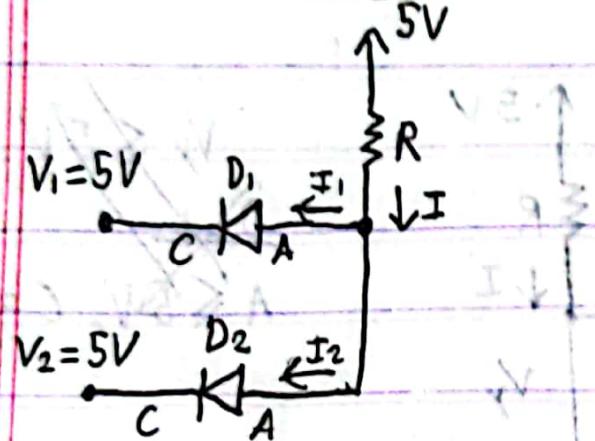

$V_Y \leq 5V$ for current to flow

$D_1:$

$A \rightarrow V_Y \leq 5V$

$C \rightarrow 5V$


$\therefore D_1 = OFF$

$D_2:$

$A \rightarrow V_Y \leq 5V$

$C \rightarrow \cancel{5V}$

$\therefore D_2 = OFF$

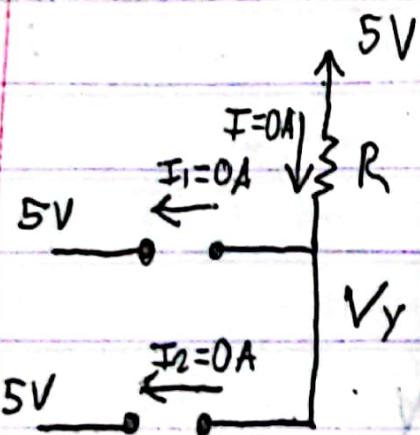

• Since D_1 and D_2 are replaced with open circuit, \therefore current flow = $0A$ so $V_A = V_C = 0.5V$, Since $V_C = V_Y$ so

$V_Y = 5V$, $V_A \geq A$

- * Min Voltage can be found out using AND gate implementation.
- * The resistor, R = Pull up resistor.

* If the voltages connected to the diode is not 0V and 5V then in order to find if the diodes are ON or OFF, cases need to be solved. For example:


- Case - 1 : $D_1 = \text{ON}$ and $D_2 = \text{ON}$
- " - 2 : $D_1 = \text{ON}$ " $D_2 = \text{OFF}$
- " - 3 : $D_1 = \text{OFF}$ " $D_2 = \text{ON}$
- " - 4 : $D_1 = \text{OFF}$ " $D_2 = \text{OFF}$

* There may be more than 2 diodes for both OR and AND operations.

* In case of OR operation choose the diode connected to the highest voltage to be ON and others to be OFF.


* In case of AND operation choose the diode connected to the lowest voltage to be ON and others to be OFF.

* E_0 : ($V_1 = 4V$ and $V_2 = 5V$) (OR)

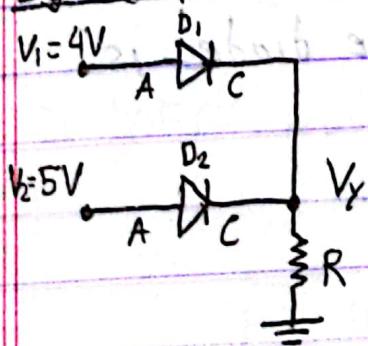

Consider,
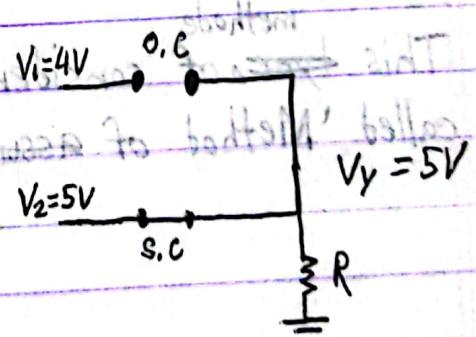
$$\begin{aligned} D_1 &= \text{OFF} \\ D_2 &= \text{ON} \end{aligned}$$



D_1 :


$$A \rightarrow V_1 = 4V$$

$$C \rightarrow V_c = 5V$$

$$\therefore V_A < V_c \text{ so OFF}$$

\therefore Consideration was correct

* Eg: ($V_1 = 0V$ and $V_2 = 1V$) (AND)

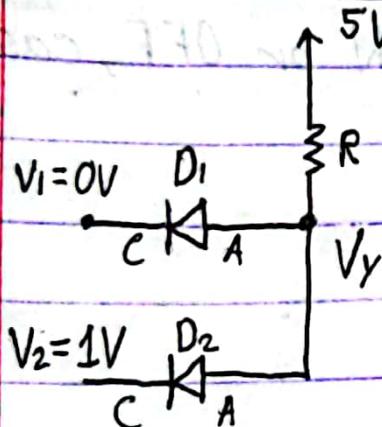


Consider,

$D_1 = ON$

$D_2 = OFF$

$V_1 = 0V$

$V_2 = 1V$

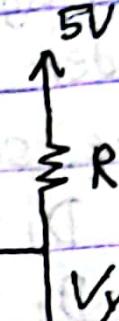

$$V_y = V_1 = 0V$$

$$A \rightarrow 0V$$

$$C = 1V$$


$V_1 < V_C$, $\therefore D_2$ is OFF, so the consideration was correct.

method


* This ~~type~~ of considering the states of the diodes is called 'Method of Assumption'.

Non-Ideal diode:


- * In real life diode a bit of power is consumed when current flows through it which is proportional to the current that passes through it ($P \propto I_d$). Therefore we can say there is also a small voltage drop across the diode when current passes through it.
- * The $P \propto I_d$ of a diode is similar to a voltage source where $P \propto I$.
- * So when the diode is in 'ON' mode we can replace it with a V-source.

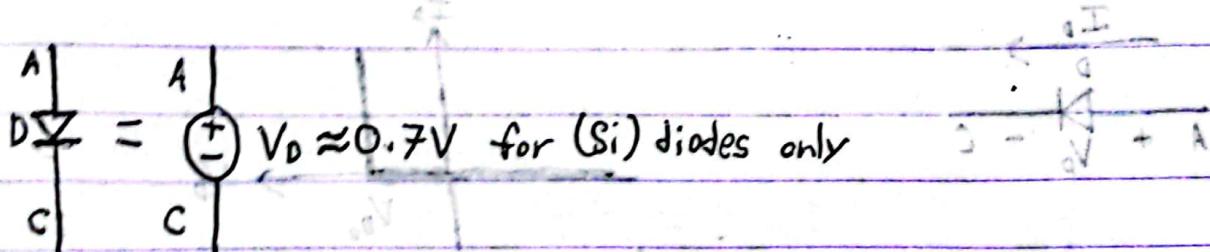


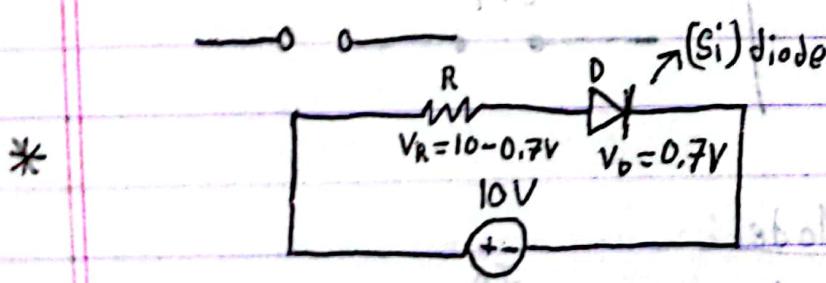
- * In 'OFF' mode the diode is still replaced with open circuit.



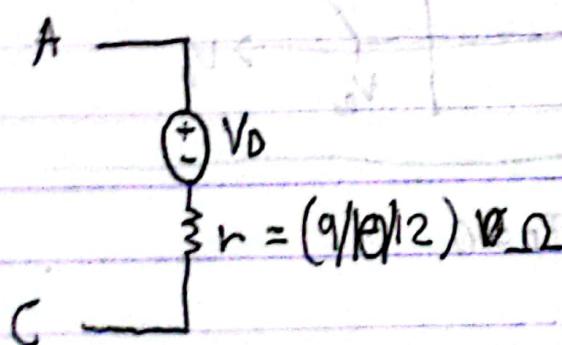- * More accurate model of Diode: (While it is ON)



Ideal Diode Model:

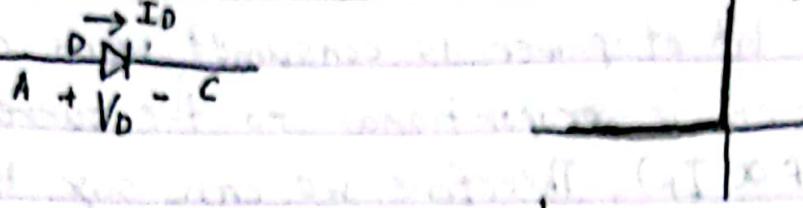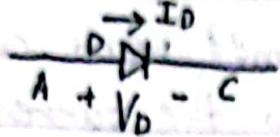

if $I_D > 0$, then $V_D = 0$



'ON'

if $V_D < 0$, then $I_D = 0$

'OFF'

State Eqn

Constant Voltage Drop (C.V.D) model:

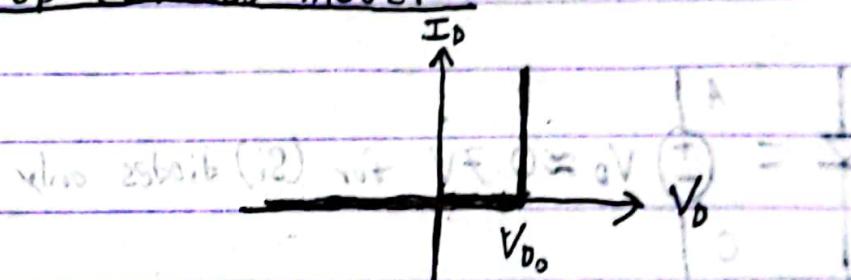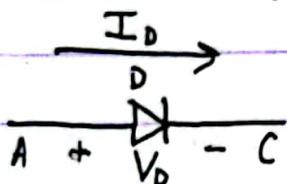

if $I_D > 0$, then $V_D = V_{D_0}$


'ON'

$V_{D_0} \approx 0.7\text{V} \rightarrow (\text{Si})\text{Diode}$

if $V_D < V_{D_0}$, then $I_D = 0$



'OFF'

V-Source + Resistance Model:

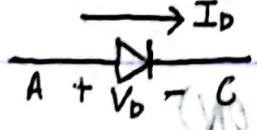

if $I_D > 0$, then $V_D = V_{D_0} + I_D r$

'ON'

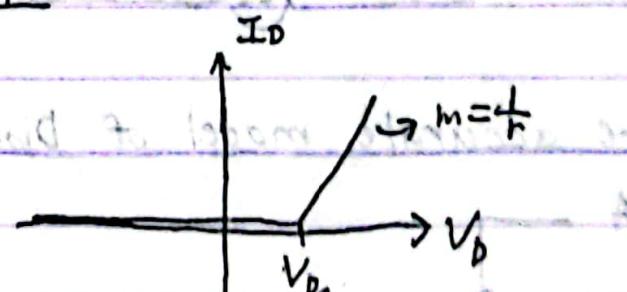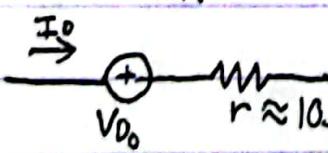


if $V_D < V_{D_0}$, then $I_D = 0$

'OFF'

* V_{D_0} = Cut in voltage

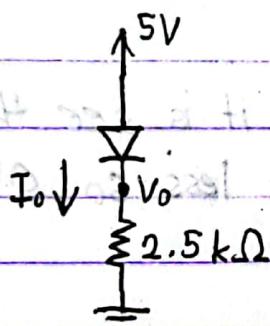- * For faster calculation use Ideal model.
- * " accurate " " Voltage + resistance model ($C.V.D + r$).
- * " bit of both " " C.V.D model.
- * C.V.D will be used mostly in this course.
- * Eg:




Find V_o and I_o using :

① Ideal diode model

② C.V.D model ($V_{D0} = 0.7V$)

③ C.V.D + r model ($V_{D0} = 0.7V$ and $r = 10\Omega$)


①

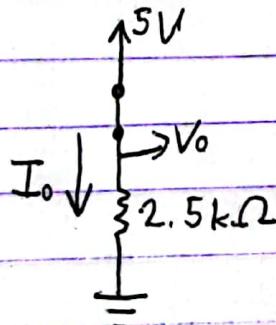

$$V_o = 5V$$

$$I_o = \frac{5-0}{2.5} = 2 \text{ mA}$$


②

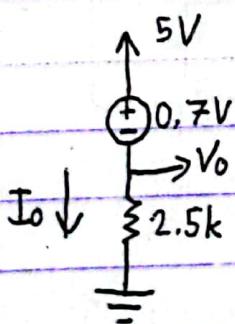

$$5 - V_o = 0.7$$

$$V_o = 4.3V$$
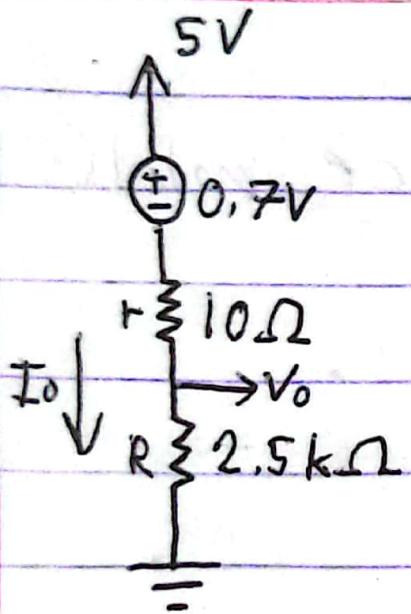
$$I_o = \frac{4.3-0}{2.5} = 1.72 \text{ mA}$$



$$K, V, L \Rightarrow 5 = 0.7 + 0.01 I_o + 2.5 I_o$$

$$\Rightarrow I_o = 1.713 \text{ mA}$$

~~$$V_o = I_o \times R$$~~

$$\therefore V_o - 0 = I_o R$$

$$V_o = 4.283 \text{ V}$$

* By comparing CVD and CVD+r models it is seen that difference in the calculated values are very less so CVD and Ideal models will be used mostly.

Real Diode:

* Are semiconductors (Si, Ge, ...)

Ease of Current Flow

Conductors Semiconductors Insulators

intrinsic (pure)

mainly used
extrinsic (impure)




(2-3) \times $P \Rightarrow$

$h \Rightarrow$



+ve charge
carriers (hole)

-ve charge
carriers (electron)

P-n Junction Diode:

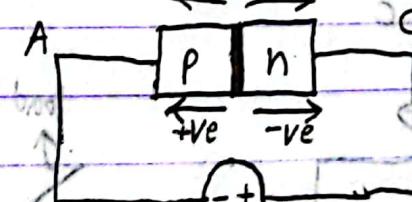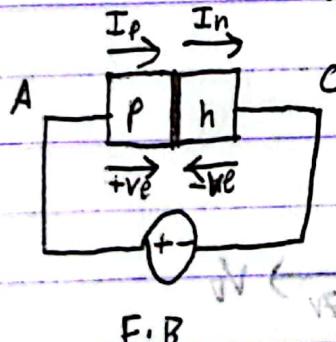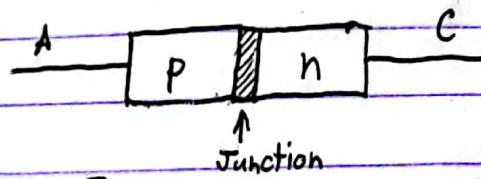

*

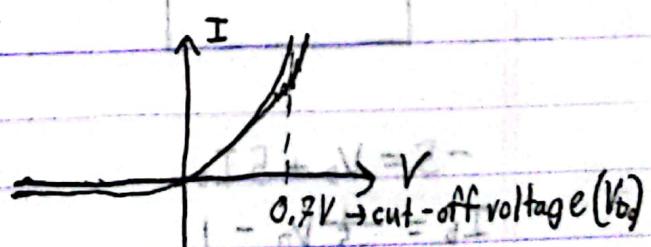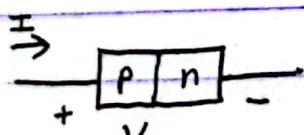


$$I = I_s (e^{\frac{V}{V_T}} - 1), I_s = \text{Reverse saturation current} = 10^{-12} \sim 10^{-9} A$$

$V_T = \text{Thermal voltage} = 0.025 V$

- I_s and V_T rises with temperature



Schottky Diode:

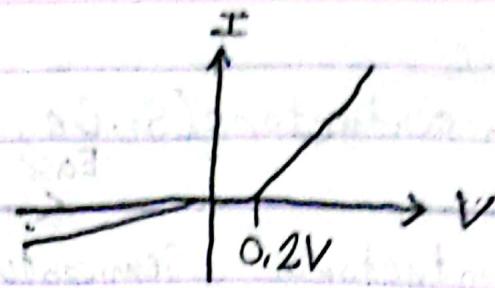

* Disadvantage

- Current is not 0 in R.B.

$$W = 4(L - 7)(V - 5)$$

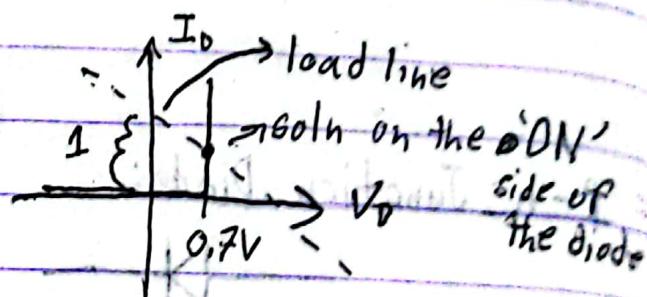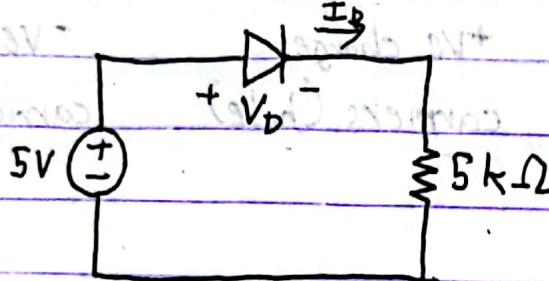


$$\text{Diode} = C, V, D,$$

$$5 = V_D + 5 I_D$$

$$I_D = -\frac{1}{5} V_D + 1 \quad \rightarrow \text{load line}$$

$$y = -m x + c$$

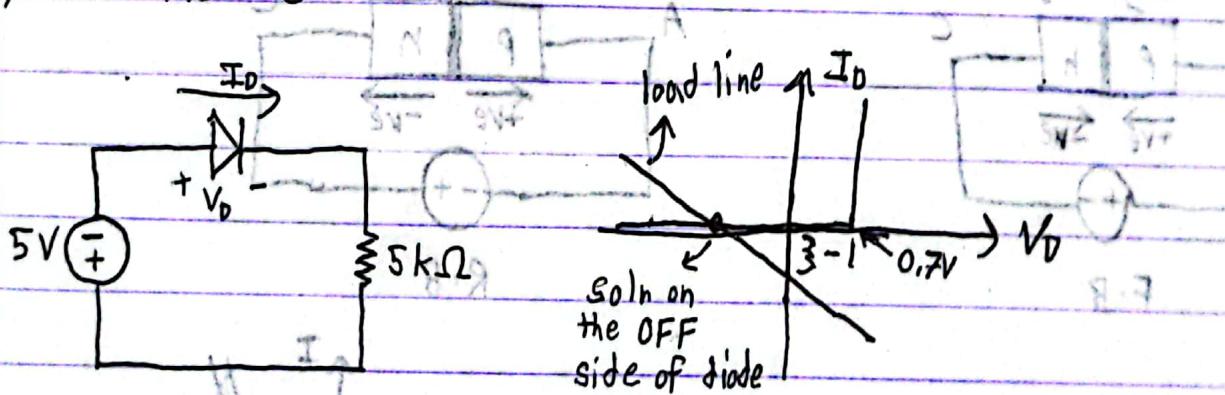

$$-5 = V_D + 5 I_D$$

$$I_D = -\frac{1}{5} V_D - 1$$

- * This approach works on simple circuits only.
- * For complex circuits the Method of assumed state is used if Diode is involved.